



## American International University- Bangladesh

Department of Electrical and Electronic Engineering

EEE 1202: Introduction to Electrical Circuits Laboratory

**Title:** Study of Superposition Theorem for DC circuit.

### Introduction:

The superposition theorem states that in a linear bilateral multi-source DC circuit, the current through or voltage across any particular element may be determined by considering the contribution of each source independently, with the remaining sources replaced with their internal resistance. The contributions are then summed, paying attention to polarities, to find the total value. Superposition cannot in general be applied to non-linear circuits or to non-linear functions such as power.

The objectives of this exercise are to-

1. investigate the application of the superposition theorem to multiple DC source circuits in terms of both voltage and current measurements.
2. examine the power measurement.

### Theory and Methodology:

The principle of superposition is applicable only for linear systems. The concept of superposition can be explained mathematically by the following response and excitation principle:

$$\begin{aligned} i_1 &\rightarrow v_1 \\ i_2 &\rightarrow v_2 \\ i_1 + i_2 &\rightarrow v_1 + v_2 \end{aligned}$$

Then, the quantity to the left of the arrow indicates the excitation and to the right, the system response. Thus, we can state that a device, if excited by a current  $i_1$  will produce a response  $v_1$ . Similarly, an excitation  $i_2$  will cause a response  $v_2$ . Then if we use an excitation  $i_1 + i_2$ , we will find a response  $v_1 + v_2$ .

The principle of superposition has the ability to reduce a complicated problem to several easier problems each containing only a single independent source.

Superposition theorem states that,

***In any linear circuit containing multiple independent sources, the current or voltage at any point in the network may be calculated as algebraic sum of the individual contributions of each source acting alone.***

When determining the contribution due to a particular independent source, we disable all the remaining independent sources. That is, all the remaining voltage sources are made zero by replacing them with short circuits, and all remaining current sources are made zero by replacing them with open circuits. Also, it is important to note that if a dependent source is present; it must remain active (unaltered) during the process of superposition.

### **Action Plan:**

- (i) In a circuit comprising of many independent sources, only one source is allowed to be active in the circuit, the rest are deactivated (turned off).


- (ii) To deactivate a voltage source, replace it with a short circuit, and to deactivate a current source, replace it with an open circuit.
- (iii) The response obtained by applying each source, one at a time, are then added algebraically to obtain a solution.

**Limitations:** Superposition is a fundamental property of linear equations and, therefore, can be applied to any effect that is linearly related to the cause. That is, we want to point out that, superposition principle applies only to the current and voltage in a linear circuit but it cannot be used to determine power because power is a non-linear function.

### Pre-Lab Homework:


Use PSpice and reference book for solving the following problem. Student must present the simulation results to the instructor before the start of the experiment.

**HW 1:** Find  $V_{out}$  using superposition theorem of Figure 6.0.

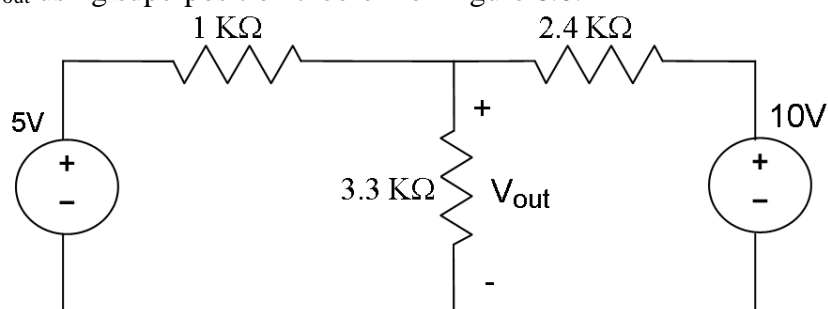

**Fig 6.0**

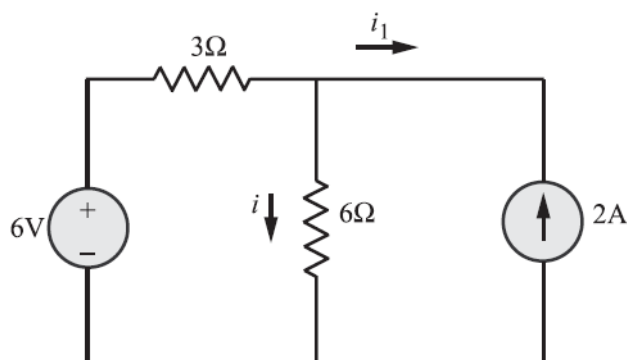**HW 2:** Find the current in the  $6\Omega$  resistor using the principle of superposition for the following circuit:



### Apparatus:

1. Trainer board
2. Digital multimeter
3. DC source
4. Resistors : 4.7k, 6.8k, 10k, 22k, 33k [1 pcs]
5. Connecting wires


### Precautions:

To consider the effect of one voltage source the other must be replaced with a wire. Simply switching off the connection does not give the correct circuit configuration.


Sometimes the ammeters don't work properly so to determine current take the voltage drop across the resistor and divide by the resistance value to obtain the current passing through that particular element or branch. Always mention the units when taking the readings or doing the calculations.

### Experimental Procedure:

#### **Circuit Diagram:**

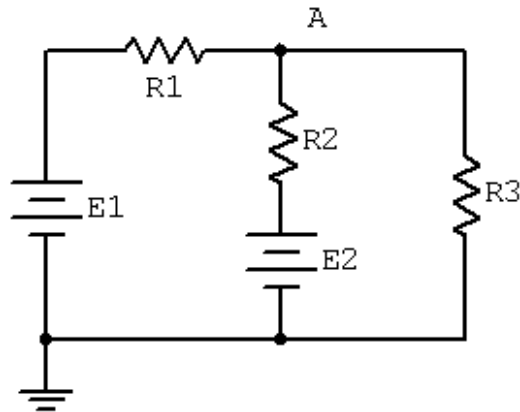

**Figure 6.1**

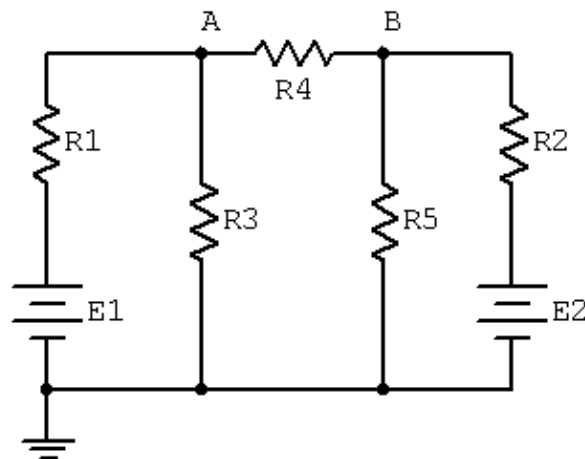

**Figure 6.2**

#### Voltage Application

1. Consider the dual supply circuit of Figure 6.1 using  $E1 = 10$  volts,  $E2 = 15$  volts,  $R1 = 4.7$  k,  $R2 = 6.8$  k and  $R3 = 10$  k. To find the voltage from node A to ground, superposition may be used. Each source is considered by itself. First consider source  $E1$  by assuming that  $E2$  is replaced with its internal resistance (a short). Determine the voltage at node A using standard series-parallel techniques and record it in Table 6.1. Make sure to indicate the polarity. Repeat the process using  $E2$  while shorting  $E1$ . Finally, sum these two voltages and record in Table 6.1.

2. To verify the superposition theorem, the process may be implemented directly by measuring the contributions. Build the circuit of Figure 6.1 with the values specified in step 1, however, replace  $E2$  with a short. Do **not** simply place a shorting wire across source  $E2$ ! This will overload the power supply.

3. Measure the voltage at node A and record in Table 6.1. Be sure to note the polarity.
4. Remove the shorting wire and insert source E2. Also, replace source E1 with a short. Measure the voltage at node A and record in Table 6.1. Be sure to note the polarity.
5. Remove the shorting wire and re-insert source E1. Both sources should now be in the circuit. Measure the voltage at node A and record in Table 6.1. Be sure to note the polarity. Determine and record the deviations between theory and experimental results.

#### Current and Power Application

6. Consider the dual supply circuit of Figure 6.2 using  $E1 = 10$  volts,  $E2 = 15$  volts,  $R1 = 4.7$  k,  $R2 = 6.8$  k,  $R3 = 10$  k,  $R4 = 22$  k and  $R5 = 33$  k. To find the current through  $R4$  flowing from node A to B, Superposition may be used. Each source is again treated independently with the remaining sources replaced with their internal resistances. Calculate the current through  $R4$  first considering  $E1$  and then considering  $E2$ . Sum these results and record the three values in Table 6.2.
7. Assemble the circuit of Figure 6.2 using the values specified. Replace source  $E2$  with a short and measure the current through  $R4$ . Be sure to note the direction of flow and record the result in Table 6.2.
8. Replace the short with source  $E2$  and swap source  $E1$  with a short. Measure the current through  $R4$ . Be sure to note the direction of flow and record the result in Table 6.2.
9. Remove the shorting wire and re-insert source  $E1$ . Both sources should now be in the circuit. Measure the current through  $R4$  and record in Table 6.2. Be sure to note the direction. Determine and record the deviations between theory and experimental results.
10. Power is not a linear function as it is proportional to the square of either voltage or current. Consequently, superposition should not yield an accurate result when applied directly to power. Based on the measured currents in Table 6.2, calculate the power in  $R4$  using  $E1$ -only and  $E2$ -only and record the values in Table 6.3. Adding these two powers yields the power as predicted by superposition. Determine this value and record it in Table 6.3. The true power in  $R4$  may be determined from the total measured current flowing through it. Using the experimental current measured when both  $E1$  and  $E2$  were active (Table 6.2), determine the power in  $R4$  and record it in Table 6.3.

#### Simulation and Measurement:

1. Calculate the voltage across and current through  $R5$  as per the superposition theorem and show all the calculations clearly.
2. Compare the simulation results with your experimental data/ wave shapes and comment on the differences (if any).

#### Instructions for report writing:

1. Describe in words what the data means.
2. Compare your experimental values or findings with the theoretical values and analyze the result.

**Data Tables:**

Source	$V_A$ Theory	$V_A$ Experimental	Deviation
E1 only			
E2 only			
E1 & E2			

**Table 6.1**

Source	$I_{R4}$ Theory	$I_{R4}$ Experimental	Deviation
E1 only			
E2 only			
E1 & E2			

**Table 6.2**

Source	$P_{R4}$
E1 only	
E2 only	
E1+E2	
E1 and E2	

**Table 6.3****Discussion:**

Determine whether or not the theorem was accepted. Discuss any mistakes you might have made while conducting the investigation and describe ways the study could have been improved.

**Conclusion:**

Summarize your experiment here and discuss whether the objectives were fulfilled or not within a short paragraph.

**Reference(s):**

1. Robert L. Boylestad, "Introductory Circuit Analysis", Prentice Hall, 12<sup>th</sup> Edition, New York, 2010, ISBN 9780137146666.