

# Chapter 5


## Series DC Circuit




## Two Elements are in Series

Two elements are in series if

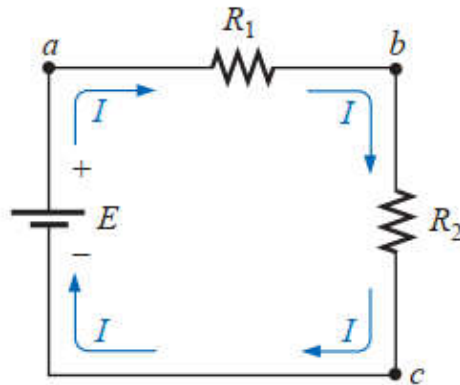
1. They have **only one terminal in common** (i.e., one lead of one is connected to only one lead of the other).
2. The common point between the two elements is **not connected to another current-carrying element**.
3. The current is the same through the two series elements.




$R_1$  and  $R_2$  are in series

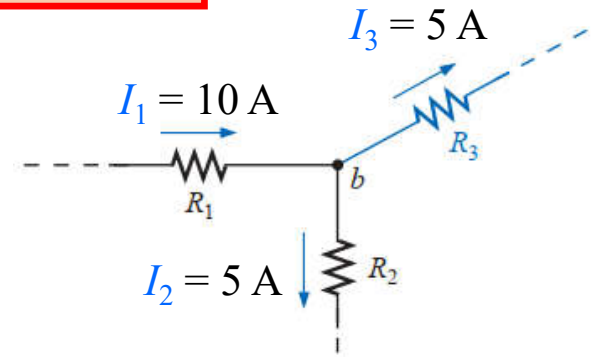

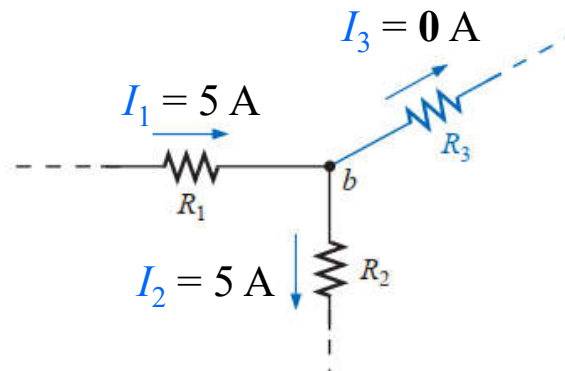$R_1$  and  $R_2$  are not in series  
 $R_2$  and  $R_3$  are not in series



$R_1$  and  $R_2$  may be in series

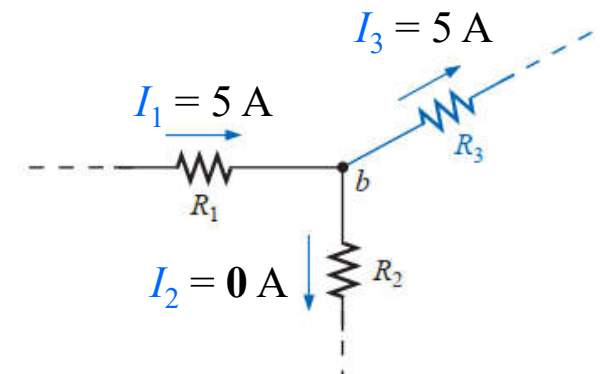

$R_1$  and  $R_3$  may be in series

## 5.2 Series Resistance

### Total or Net or Effective Resistance of a Series Circuit or a Branch:


- ❖ The total resistance of a series configuration is the sum of the value of individual resistance, that is Eq. (5.1).
- ❖ The more resistors we add in series, the greater the resistance, no matter what their value.
- ❖ The total resistance greater than the value of all the individual resistance, that is Eq. (5.1.1).
- ❖ The total resistance of  $n$  resistors of the same value in series is simply *multiply the value of one of the resistors by the number in series*; that is as Eq. (5.2)

$$R_T = R_{eff} = R_1 + R_2 + R_3 + \dots + R_n \quad (5.1)$$


If  $R_1 = R_2 = R_3 = \dots = R_n = R$

$$R_T = R_{eff} = nR \quad (5.2)$$

$$R_T > R_1; R_T > R_2; \dots, R_T > R_N \quad (5.1.1)$$

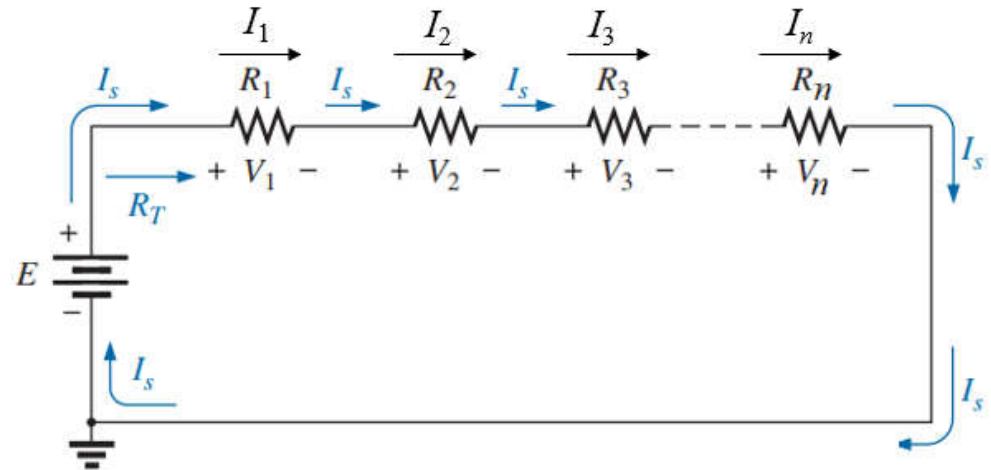

**EXAMPLE 5.1** Determine the total resistance of the series connection in Fig. 5.6. Note that all the resistors appearing in this network are standard values.

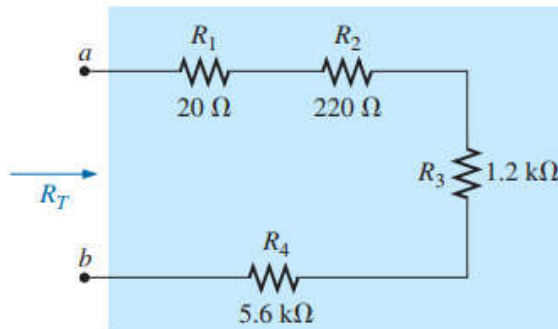

**FIG. 5.6**


*Series connection of resistors for Example 5.1.*

**Solution:** Note in Fig. 5.6 that even though resistor  $R_3$  is on the vertical and resistor  $R_4$  returns at the bottom to terminal  $b$ , all the resistors are in series since there are only two resistor leads at each connection point.

Applying Eq. (5.1):

$$\begin{aligned} R_T &= R_1 + R_2 + R_3 + R_4 \\ R_T &= 20\ \Omega + 220\ \Omega + 1.2\ \text{k}\Omega + 5.6\ \text{k}\Omega \\ \text{and } R_T &= 7040\ \Omega = \mathbf{7.04\ \text{k}\Omega} \end{aligned}$$

**EXAMPLE 5.2** Find the total resistance of the series resistors in Fig. 5.7. Again, recognize  $3.3\ \text{k}\Omega$  as a standard value.

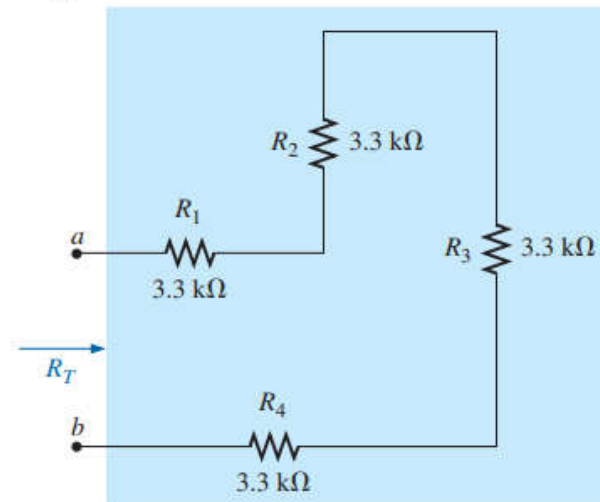

**FIG. 5.7**

*Series connection of four resistors of the same value (Example 5.2).*


**Solution:** Again, don't be concerned about the change in configuration. Neighboring resistors are connected only at one point, satisfying the definition of series elements.

$$\begin{aligned} \text{Eq. (5.2): } R_T &= NR \\ &= (4)(3.3\ \text{k}\Omega) = \mathbf{13.2\ \text{k}\Omega} \end{aligned}$$


**Practice Book Problem [5.2 Series Resistance] Problems: 1, 2, 5, 6**

## Test Your Knowledge

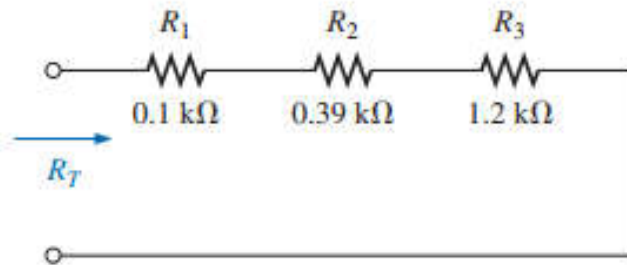
2. Find the total resistance  $R_T$  for each configuration in Fig. 5.86. Note that only standard resistor values were used.




(a)

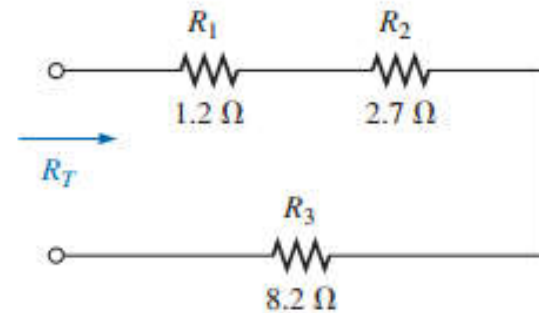

(b)

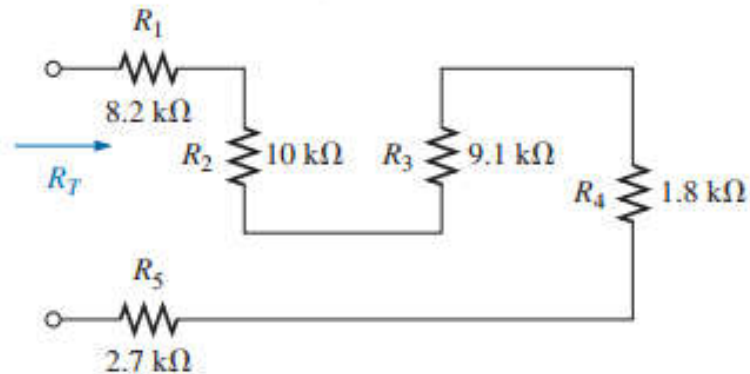

(c)



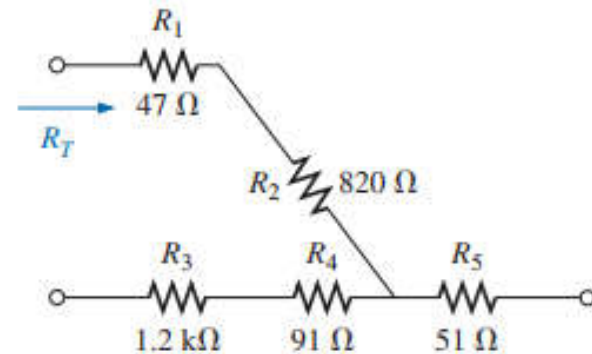


(d)




**FIG. 5.86** Problem 2.
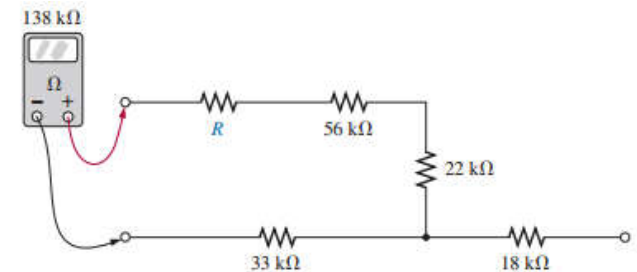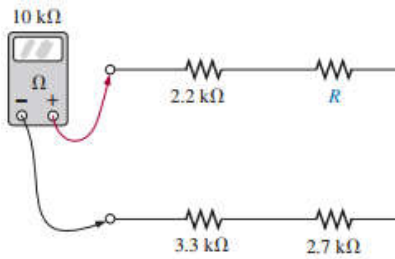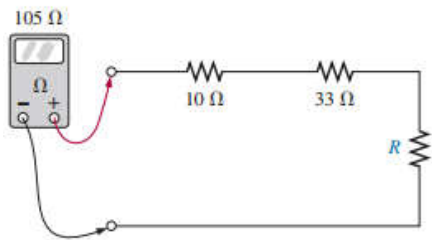
## Test Your Knowledge

What is the value of  $R$  for the following cases of the reading of **OHM METER**?



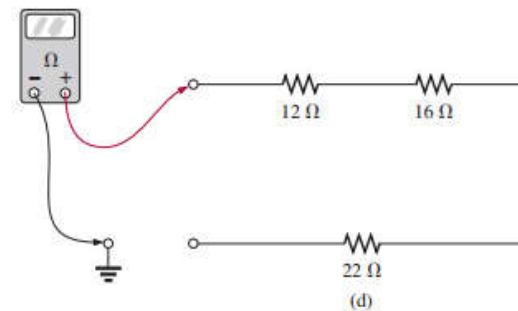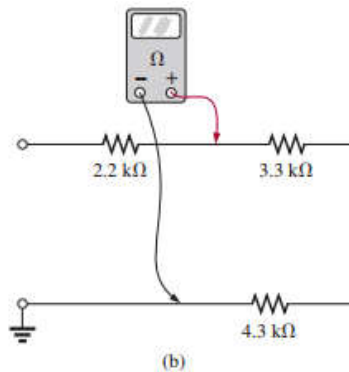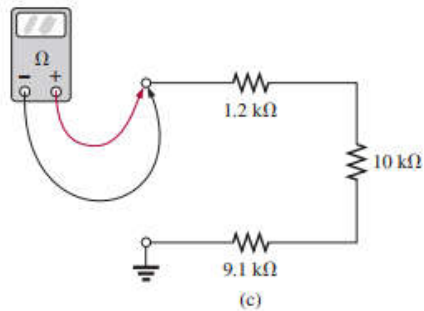What is the reading of **OHM METER** for the following cases?



## 5.3 Series Circuit

A **series circuit** is one in which several resistances are connected one after the other.

**Current in a series circuit:** The current is the same at every point in a series circuit, that is as following equation for the following circuit.


$$I_1 = I_2 = I_3 = \dots = I_n = I_s$$

**Current Calculation of a series circuit:** According ohm's law, the current of the following circuit is as follows:

$$I_s = \frac{E}{R_T} \quad (\text{A}) \quad (5.3)$$

**Voltage drop across individual resistance in a series circuit :** According ohm's law, the of the following circuit is as follows:
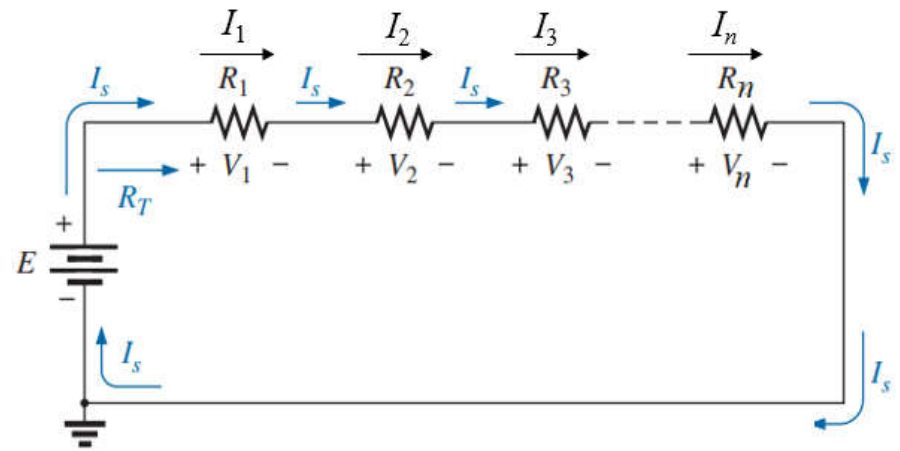
$$\begin{array}{ll} V_1 = I_1 R_1 = I_s R_1 & V_2 = I_2 R_2 = I_s R_2 \\ V_3 = I_3 R_3 = I_s R_3 & \dots \dots \dots V_n = I_n R_n = I_n R_2 \end{array} \quad (\text{V}) \quad (5.4)$$









If  $R_1 = R_2 = R_3 = \dots = R_n = R$

$$V_1 = V_2 = V_3 = \dots = V_n = \frac{E}{n}$$



## Different Ways to Sketch the Same Series Circuit

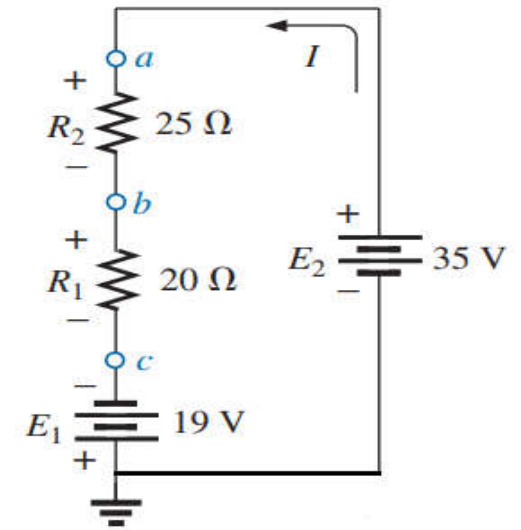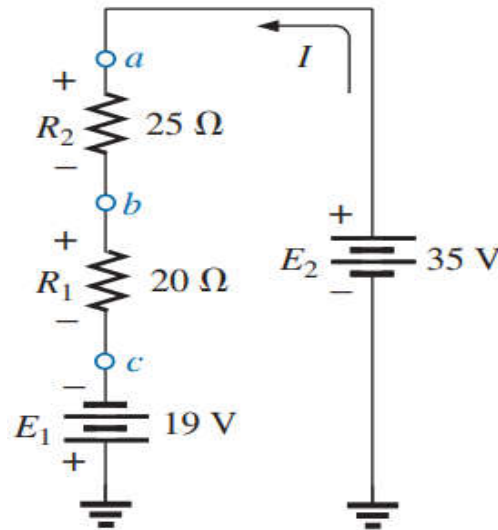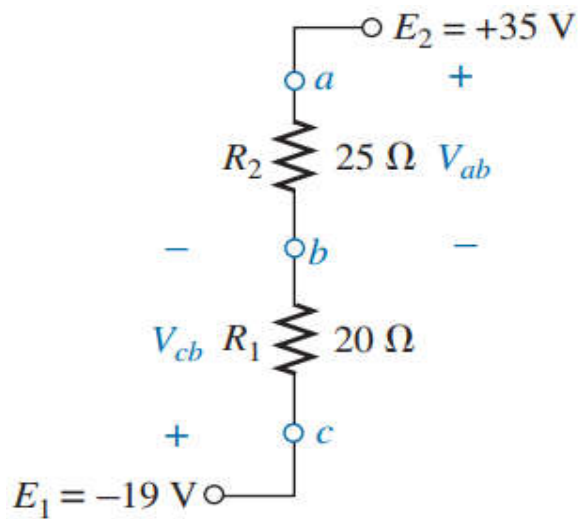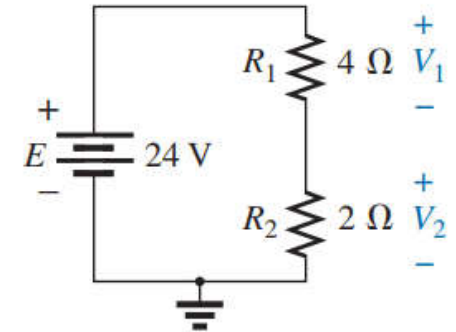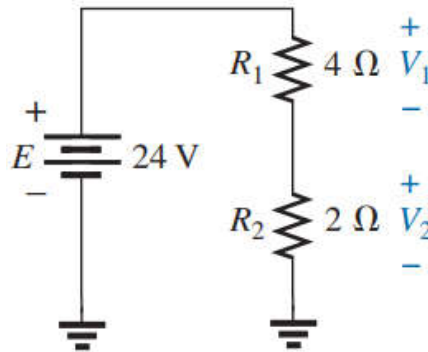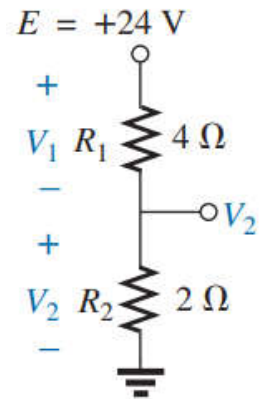



**EXAMPLE 5.4** For the series circuit in Fig. 5.15:


- Find the total resistance  $R_T$ .
- Calculate the resulting source current  $I_s$ .
- Determine the voltage across each resistor.

**Solutions:**

$$\begin{aligned} \text{a. } R_T &= R_1 + R_2 + R_3 \\ &= 2\ \Omega + 1\ \Omega + 5\ \Omega \\ R_T &= \mathbf{8\ \Omega} \end{aligned}$$

$$\text{b. } I_s = \frac{E}{R_T} = \frac{20\ \text{V}}{8\ \Omega} = \mathbf{2.5\ \text{A}}$$

$$\begin{aligned} \text{c. } V_1 &= I_1 R_1 = I_s R_1 = (2.5\ \text{A})(2\ \Omega) = \mathbf{5\ \text{V}} \\ V_2 &= I_2 R_2 = I_s R_2 = (2.5\ \text{A})(1\ \Omega) = \mathbf{2.5\ \text{V}} \\ V_3 &= I_3 R_3 = I_s R_3 = (2.5\ \text{A})(5\ \Omega) = \mathbf{12.5\ \text{V}} \end{aligned}$$

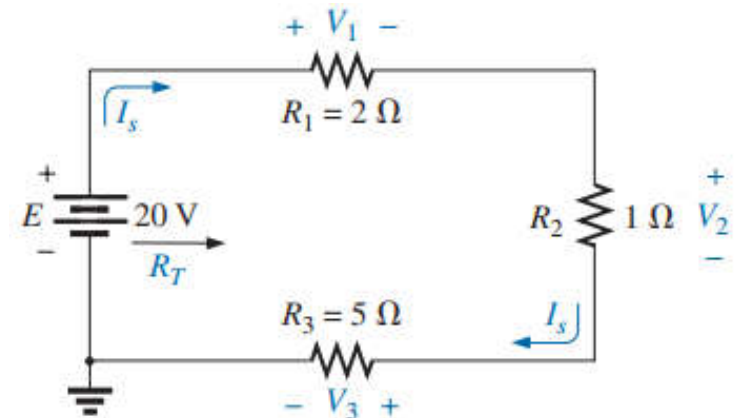

**FIG. 5.15**

*Series circuit to be investigated in Example 5.4.*

**EXAMPLE 5.6** Given  $R_T$  and  $I_3$ , calculate  $R_1$  and  $E$  for the circuit in Fig. 5.18.

**Solution:** Since we are given the total resistance, it seems natural to first write the equation for the total resistance and then insert what we know.

$$R_T = R_1 + R_2 + R_3$$

We find that there is only one unknown, and it can be determined with some simple mathematical manipulations. That is,


$$12 \text{ k}\Omega = R_1 + 4 \text{ k}\Omega + 6 \text{ k}\Omega = R_1 + 10 \text{ k}\Omega$$

and  $12 \text{ k}\Omega - 10 \text{ k}\Omega = R_1$

so that  $R_1 = 2 \text{ k}\Omega$

The dc voltage can be determined directly from Ohm's law.

$$E = I_s R_T = I_3 R_T = (6 \text{ mA})(12 \text{ k}\Omega) = 72 \text{ V}$$

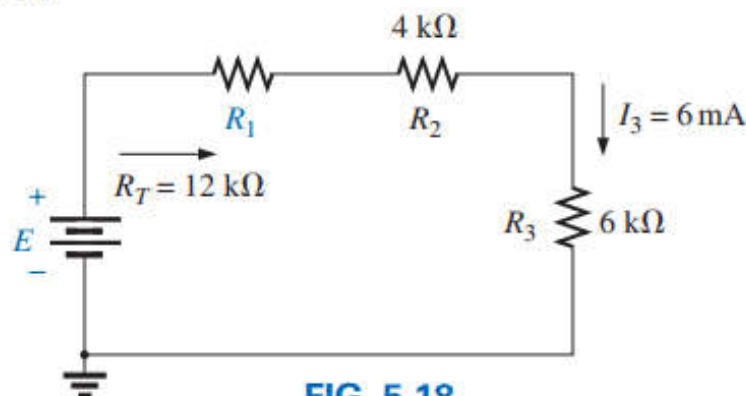

**FIG. 5.18**

*Series circuit to be analyzed in Example 5.6.*

**Practice Book Problem [5.3 Series Circuit] Problems: 7 to 11**



## 5.7 Voltage Division in Series Circuit

### Voltage Divider Rule (VDR)

**Voltage drop** across individual resistance in a **series circuit** : According ohm's law, the of the following circuit is as follows:

$$V_1 = I_s R_1 = \left( \frac{E}{R_T} \right) R_1 = \frac{R_1}{R_T} E \quad (5.7.1)$$

$$V_2 = I_s R_2 = \left( \frac{E}{R_T} \right) R_2 = \frac{R_2}{R_T} E \quad (5.7.2)$$


$$V_3 = I_s R_3 = \left( \frac{E}{R_T} \right) R_3 = \frac{R_3}{R_T} E \quad (5.7.3)$$

$$V_n = I_s R_n = \left( \frac{E}{R_T} \right) R_n = \frac{R_n}{R_T} E \quad (5.7.n)$$

Based on the Eq. (5.7.1) to (5.7.n), a general equation can be written as follows:

$$V_x = R_x \frac{E}{R_T} = \frac{R_x}{R_T} E \quad (5.10)$$

**Voltage Divider Rule (VDR):** The voltage across a resistor in a series circuit is equal to the value of that resistor ( $R_x$ ) times the total applied voltage ( $E$ ) divided by the total resistance ( $R_T$ ) of the series configuration.

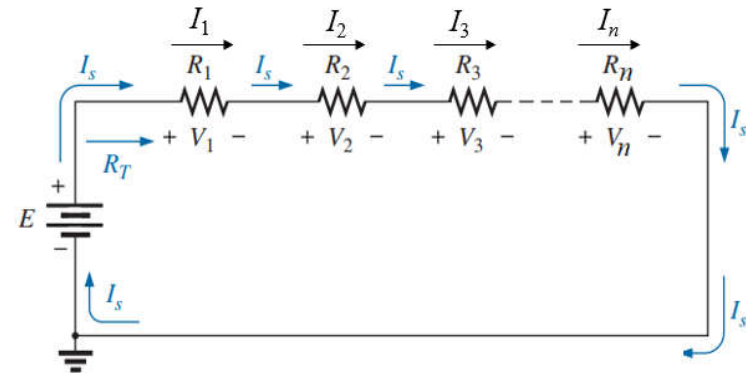

**EXAMPLE 5.16** Using the voltage divider rule, determine voltages  $V_1$ ,  $V_2$  and  $V_3$  for the series circuit in **Fig. 5.38**.


**Solution:**

$$\begin{aligned} R_T &= R_1 + R_2 + R_3 \\ &= 2 \text{ k}\Omega + 5 \text{ k}\Omega + 8 \text{ k}\Omega \\ &= 15 \text{ k}\Omega \end{aligned}$$

$$V_1 = R_1 \frac{E}{R_T} = 2 \text{ k}\Omega \left( \frac{45 \text{ V}}{15 \text{ k}\Omega} \right) = \mathbf{6 \text{ V}}$$

$$V_2 = R_2 \frac{E}{R_T} = 5 \text{ k}\Omega \left( \frac{45 \text{ V}}{15 \text{ k}\Omega} \right) = \mathbf{15 \text{ V}}$$
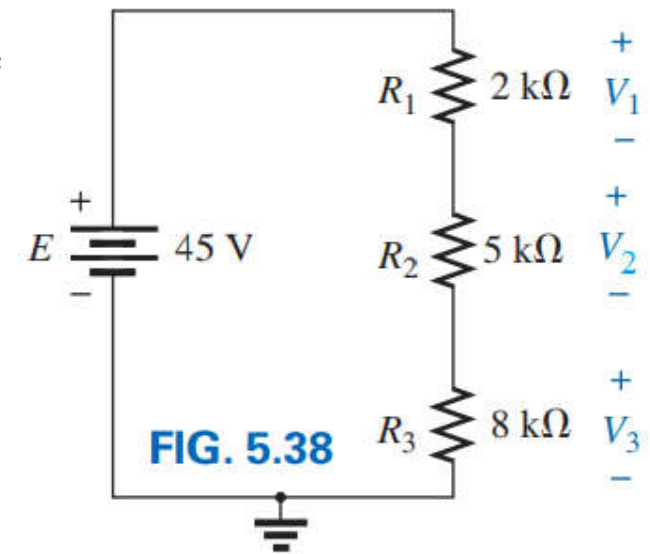
$$V_3 = R_3 \frac{E}{R_T} = 8 \text{ k}\Omega \left( \frac{45 \text{ V}}{15 \text{ k}\Omega} \right) = \mathbf{24 \text{ V}}$$



**Practice Book Problem [5.7 Voltage Divider Rule] Problems: 24, 25 and 26**

**EXAMPLE 5.7.1:** Using the voltage divider rule, determine voltages  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_{12}$  and  $V_{23}$  for the following series circuit.


**Solution:**  $R_T = R_1 + R_2 + R_3$   
 $= 100\ \Omega + 1\ \text{k}\Omega + 8.2\ \text{k}\Omega = 9.3\ \text{k}\Omega$

$$V_1 = R_1 \frac{E}{R_T} = 100\ \Omega \left( \frac{60\ \text{V}}{9.3\ \text{k}\Omega} \right) = \mathbf{0.65\ \text{V}}$$

$$V_2 = R_2 \frac{E}{R_T} = 1\ \text{k}\Omega \left( \frac{60\ \text{V}}{9.3\ \text{k}\Omega} \right) = \mathbf{6.45\ \text{V}}$$

$$V_3 = R_3 \frac{E}{R_T} = 8.2\ \text{k}\Omega \left( \frac{60\ \text{V}}{9.3\ \text{k}\Omega} \right) = \mathbf{52.9\ \text{V}}$$

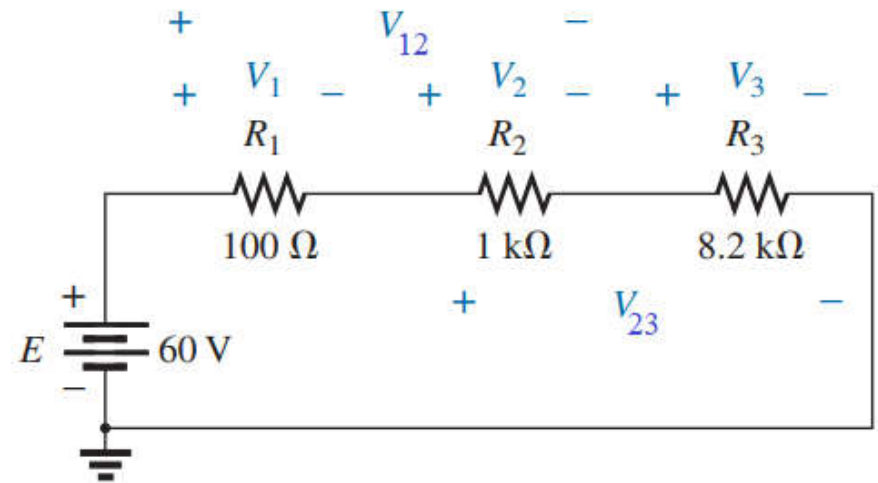$V_{12}$  is the voltage drop across the series combination of  $R_1$  and  $R_2$  and  $V_{23}$  is the voltage drop across the series combination of  $R_2$  and  $R_3$ .



$$R_{12} = R_1 + R_2 = 100\ \Omega + 1\ \text{k}\Omega = 1.1\ \text{k}\Omega$$

$$R_{23} = R_2 + R_3 = 1\ \text{k}\Omega + 8.2\ \text{k}\Omega = 9.2\ \text{k}\Omega$$

$$V_{12} = R_{12} \frac{E}{R_T} = 1.1\ \text{k}\Omega \left( \frac{60\ \text{V}}{9.3\ \text{k}\Omega} \right) = \mathbf{7.1\ \text{V}}$$

$$V_{23} = R_{23} \frac{E}{R_T} = 9.2\ \text{k}\Omega \left( \frac{60\ \text{V}}{9.3\ \text{k}\Omega} \right) = \mathbf{59.35\ \text{V}}$$

## 5.6 KIRCHHOFF'S VOLTAGE LAW (KVL)

### Statement:

(1) The algebraic sum of the potential rises and drops around a closed path (or closed loop) is zero.

OR

(2) The sum of the applied or supplied or rise voltage of a series dc circuit will equal the sum of the voltage drops of the circuit.

According to Statement (1):

$$\sum_{\text{C}} V = 0$$

(Kirchhoff's voltage law in symbolic form) (5.8)


$$E_1 - V_1 - V_2 - V_3 + E_2 = 0$$

According to Statement (2):

$$\sum_{\text{C}} V_{\text{rises}} = \sum_{\text{C}} V_{\text{drops}}$$

(5.9)

$$E_1 + E_2 = V_1 + V_2 + V_3$$

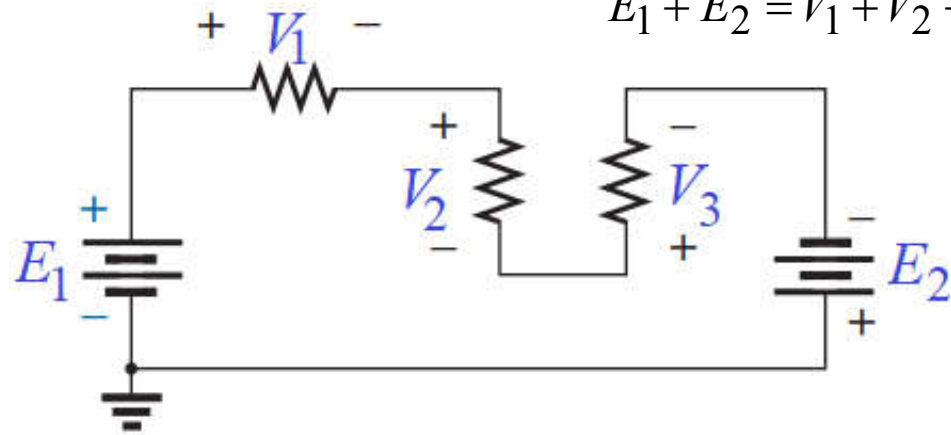



**EXAMPLE 5.8** Use Kirchhoff's voltage law to determine the unknown voltage ( $V_1$ ) for the circuit in Fig. 5.27.

**Solution:** Let considered current ( $I$ ) make closed path by flowing in clockwise (CW) direction.

$I$  is entering through **negative** terminal of  $E_1$ .

Now, let  $E_1$  is **positive**.

$I$  is entering through **positive** terminal of  $V_1$ .


So  $V_1$  is **negative**.

$I$  is entering through **positive** terminal of 4.2 V.

So 4.2 V is **negative**.

$I$  is entering through **positive** terminal of  $E_2$ .

So  $E_2$  is **negative**.

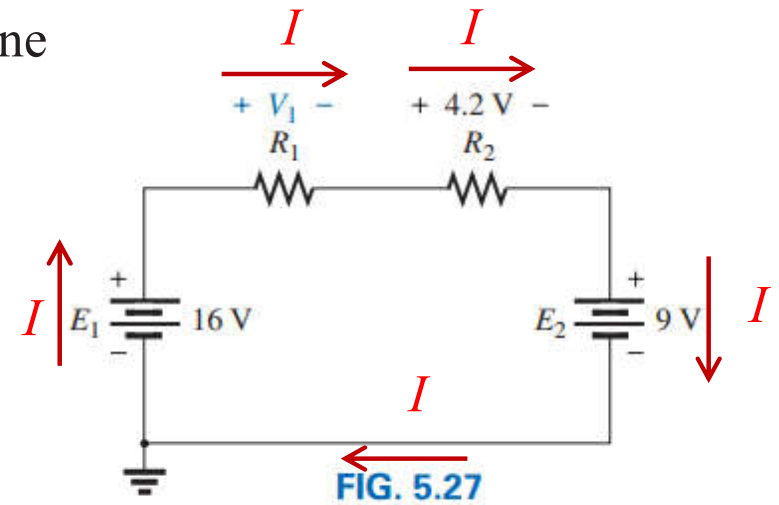

Series circuit to be examined in Example 5.8.

According to KVL we have:

$$+ E_1 - V_1 - 4.2\text{V} - E_2 = 0$$

$$V_1 = E_1 - 4.2\text{V} - E_2$$

$$\begin{aligned} V_1 &= 16\text{ V} - 4.2\text{ V} - 9\text{ V} \\ &= 2.8\text{ V} \end{aligned}$$



**EXAMPLE 5.9** Determine the unknown voltage for the circuit in Fig. 5.28.

**Solution:** This problem can be solved by two ways.

**First way:** Apply KVL around a path, including the source  $E$  and  $R_1$  (as **Loop 1**).


$$+ E_1 - 12\text{V} - V_x = 0$$

$$V_x = E_1 - 12\text{V} = 22\text{V} - 12\text{V} = \mathbf{20\text{ V}}$$

**Second way:** Apply KVL around a path, including the  $R_2$  and  $R_3$  (as **Loop 2**).

$$+ V_x - 6\text{V} - 14\text{V} = 0$$

$$V_x = 6\text{V} + 14\text{V} = \mathbf{20\text{ V}}$$

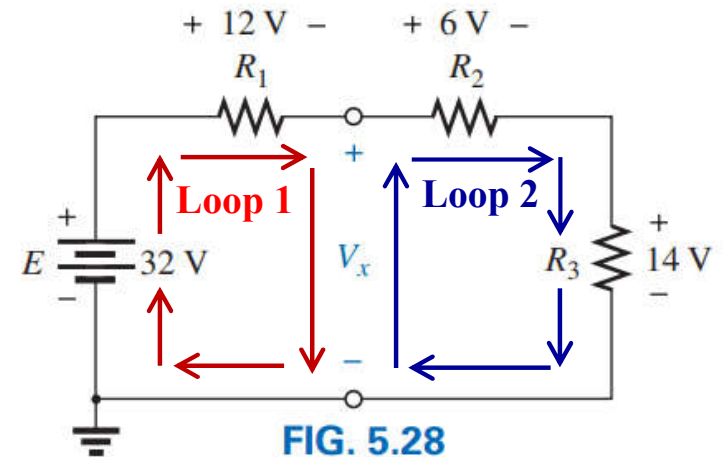

**EXAMPLE 5.6.1** Determine the unknown voltages for the following circuit.

**Solution:** Apply KVL in **Loop 1**:


$$+ E_1 - 10\text{V} - V_1 = 0$$

$$V_1 = E_1 - 10\text{V} = 24\text{V} - 10\text{V} = \mathbf{14\text{ V}}$$

Apply KVL in **Loop 2**:

$$+ E_2 + 10\text{V} - V_2 = 0$$
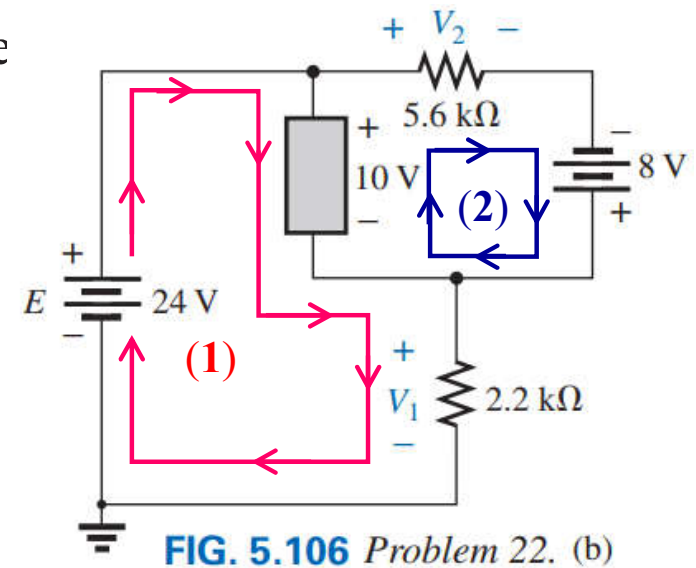
$$V_2 = E_2 + 10\text{V} = 8\text{V} + 10\text{V} = \mathbf{18\text{ V}}$$



**Practice Book Problem [SECTION 5.6 Kirchhoff's Voltage Law] Problems: 20 to 23**



## 5.4 Power Distribution in a Series Circuit

In any electrical system, the power supplied or applied or delivered will equal the power dissipated or absorbed or consumed.

$$P_E = P_{R_1} + P_{R_2} + P_{R_3} \quad (5.5)$$

$$P_E = EI_s \quad (\text{watts, W}) \quad (5.6)$$

$$P_1 = V_1 I_1 = I_1^2 R_1 = \frac{V_1^2}{R_1} = V_1 I_s = I_s^2 R_1$$

$$P_2 = V_2 I_2 = I_2^2 R_2 = \frac{V_2^2}{R_2} = V_2 I_s = I_s^2 R_2$$

$$P_3 = V_3 I_3 = I_3^2 R_3 = \frac{V_3^2}{R_3} = V_3 I_s = I_s^2 R_3$$

(W) (5.7)


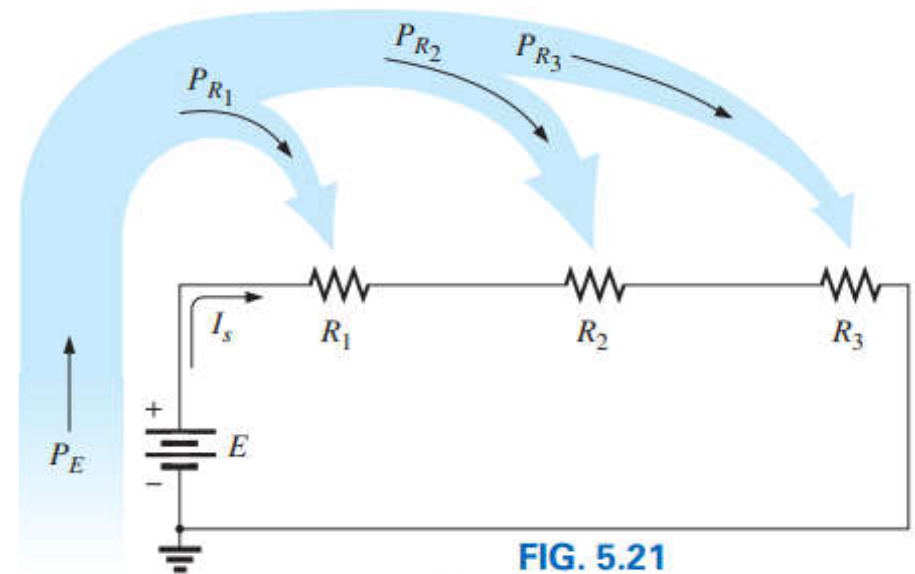


FIG. 5.21

Power distribution in a series circuit.

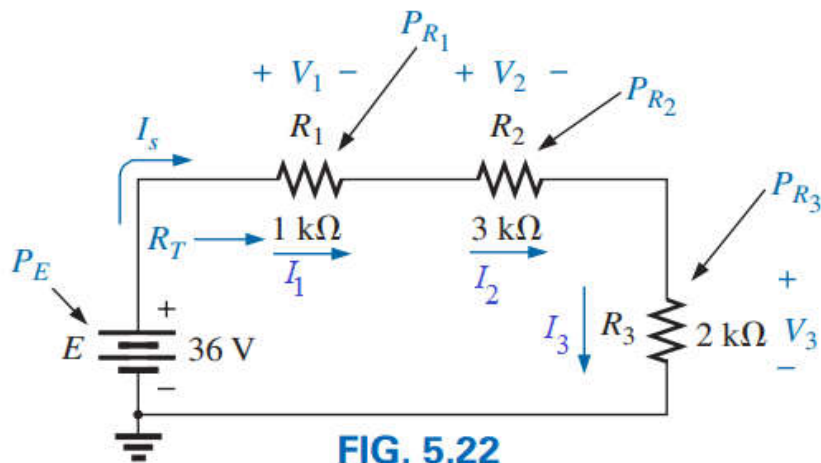**EXAMPLE 5.7** For the series circuit in Fig. 5.22 (all standard values):

- Determine the total resistance  $R_T$ .
- Calculate the current  $I_s$ .
- Determine the voltage across each resistor.
- Find the power supplied by the battery.
- Verify Kirchhoff's Voltage Law (KVL).
- Determine the power dissipated by each resistor.
- Comment on whether the total power supplied equals the total power dissipated.



Series circuit to be investigated in Example 5.7.

**Solution:**

$$(a) \quad R_T = R_1 + R_2 + R_3 = 1\text{ k}\Omega + 3\text{ k}\Omega + 2\text{ k}\Omega = \mathbf{6\text{ k}\Omega}$$

$$(b) \quad I_s = I_1 = I_2 = I_3 = \frac{E}{R_T} = \frac{36\text{ V}}{6\text{ k}\Omega} = \mathbf{6\text{ mA}}$$

$$(c) \quad V_1 = R_1 \frac{E}{R_T} = I_1 R_1 = I_s R_1 = (6\text{ mA})(1\text{ k}\Omega) = \mathbf{6\text{ V}}$$

$$V_2 = R_2 \frac{E}{R_T} = I_2 R_2 = I_s R_2 = (6\text{ mA})(3\text{ k}\Omega) = \mathbf{18\text{ V}}$$

$$V_3 = R_3 \frac{E}{R_T} = I_3 R_3 = I_s R_3 = (6\text{ mA})(2\text{ k}\Omega) = \mathbf{12\text{ V}}$$

$$(d) \quad V_1 + V_2 + V_3 = 6\text{ V} + 18\text{ V} + 12\text{ V} = \mathbf{36\text{ V} = E} \quad [\text{Verified}]$$

$$(e) \quad P_E = I_s^2 R_T = \frac{E^2}{R_T} = EI_s = (36\text{ V})(6\text{ mA}) = \mathbf{216\text{ mW}}$$

**EXAMPLE 5.7** For the series circuit in Fig. 5.22 (all standard values):

- f. Determine the power dissipated by each resistor.
- g. Comment on whether the total power supplied equals the total power dissipated.

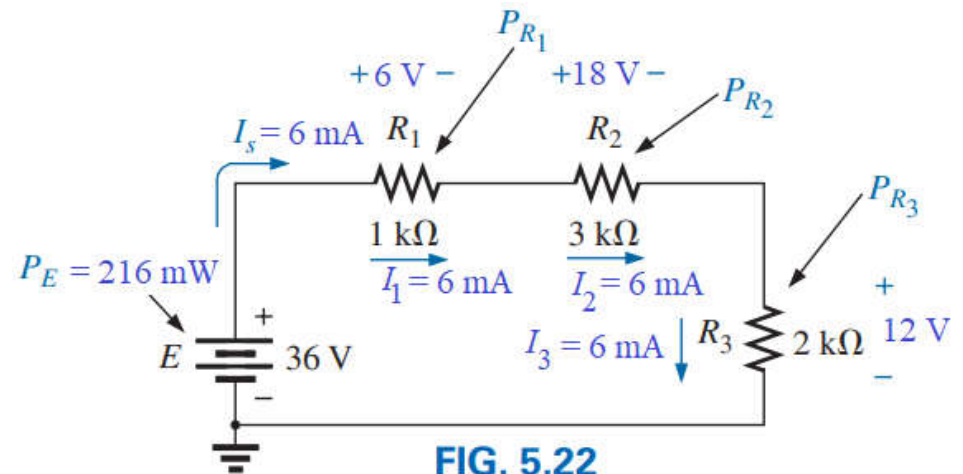


FIG. 5.22 Series circuit to be investigated in Example 5.7.

**Solution:**

$$(e) \quad P_{R1} = I_1^2 R_1 = I_s^2 R_1 = V_1 I_1 = \frac{V_1^2}{R_1} = V_1 I_s = (6 \text{ V})(6 \text{ mA}) = \mathbf{36 \text{ mW}}$$

$$P_{R2} = I_s^2 R_2 = V_2 I_2 = V_2 I_s = \frac{V_2^2}{R_2} = I_2^2 R_2 = (6 \text{ mA})^2 (3 \text{ k}\Omega) = \mathbf{108 \text{ mW}}$$


$$P_{R3} = I_s^2 R_3 = V_3 I_3 = V_3 I_s = \frac{V_3^2}{R_3} = \frac{(12 \text{ V})^2}{2 \text{ k}\Omega} = \mathbf{72 \text{ mW}}$$

$$(f) \quad \begin{aligned} P_E &= P_{R1} + P_{R2} + P_{R3} \\ &= 36 \text{ mW} + 108 \text{ mW} + 72 \text{ mW} \\ &= \mathbf{216 \text{ mW}} \text{ (Checked)} \end{aligned}$$

**Practice Book Problem [5.4 Power Distribution] Problems: 12 to 16**

## Single-Subscript Notation of Voltage

A single-subscript notation of voltage used to provide the voltage at a point with respect to ground.

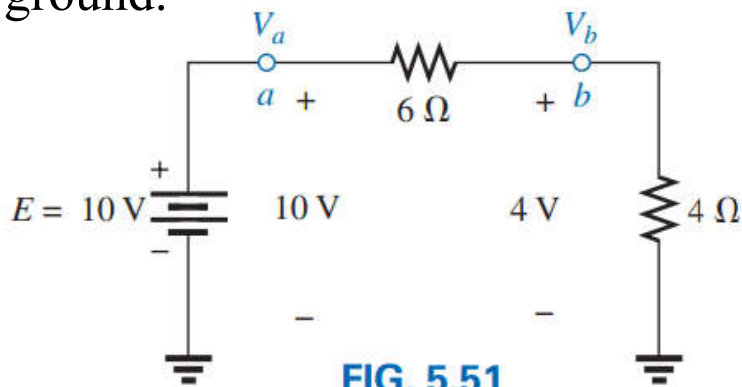

**FIG. 5.51**

*Defining the use of single-subscript notation for voltage levels.*

In Fig. 5.51:


$V_a$  is the voltage from point **a** to **ground**. In this case, it is obviously 10 V since it is right across the source voltage  $E$ . i.e.  $V_a = E = 10 \text{ V}$ .

$V_b$  is the voltage from point **b** to **ground**. Because it is directly across the  $4 \Omega$  resistor,  $V_b = 4 \text{ V}$ .

Here,  $V_{ab} = V_a - V_b = 6 \text{ V}$        $V_{ba} = V_b - V_a = -6 \text{ V}$

**EXAMPLE 5.25** Determine  $V_{ab}$ ,  $V_{cb}$ , and  $V_c$  for the network in Fig. 5.59.




**Solution:**

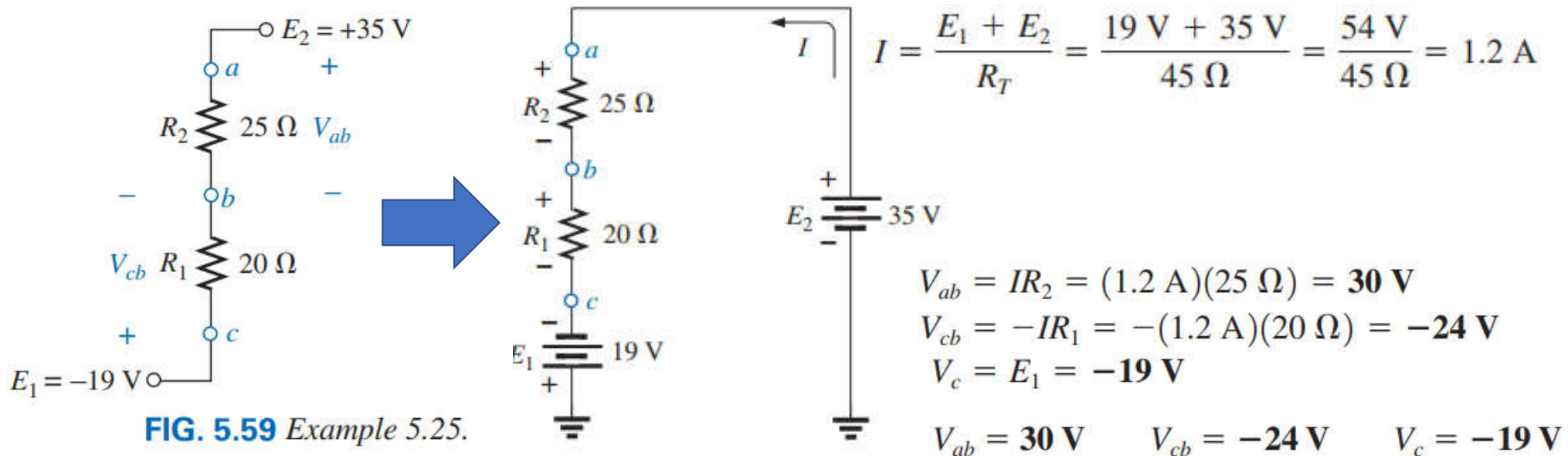

**FIG. 5.59** Example 5.25.



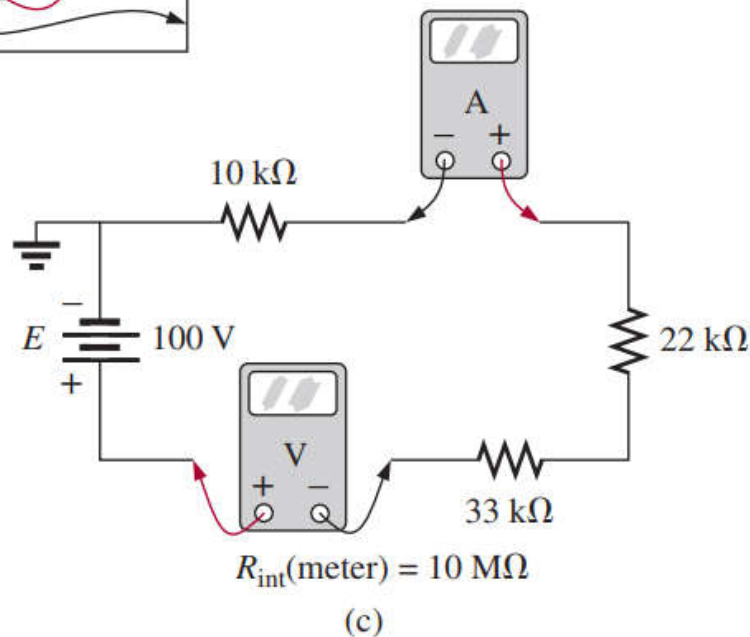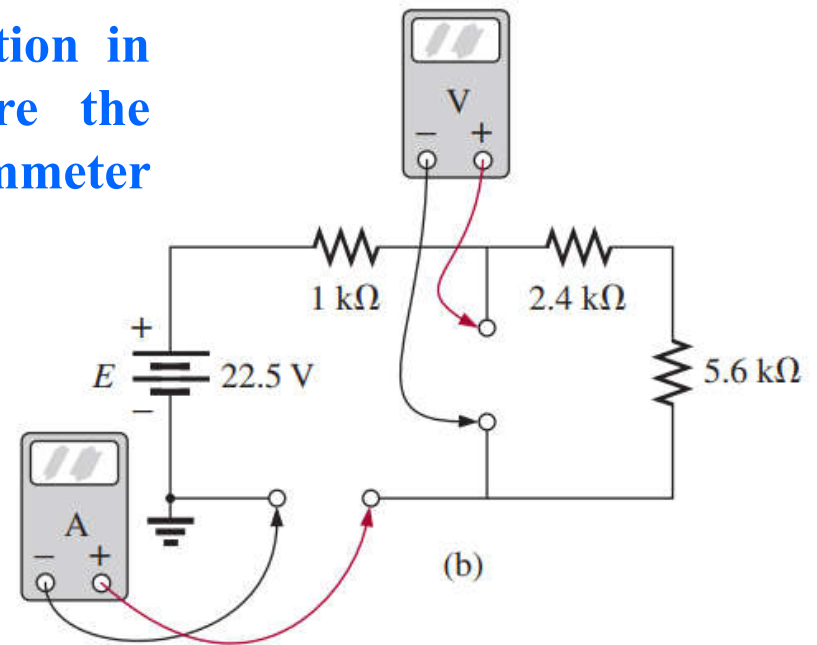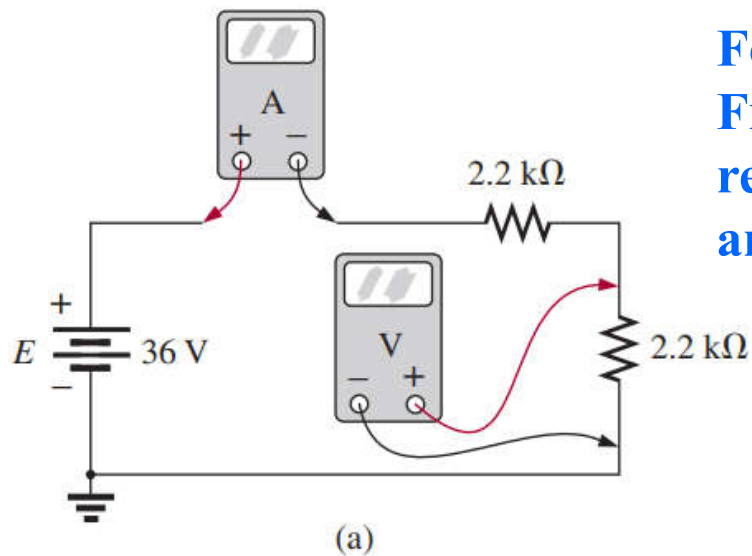
For each configuration in Fig. 5.95, what are the readings of the ammeter and the voltmeter?



## VOLTAGE SOURCES IN SERIES

Voltage sources can be connected in series.


The voltage sources to be connected in series must have same current ratings through their voltage rating may be same or different.

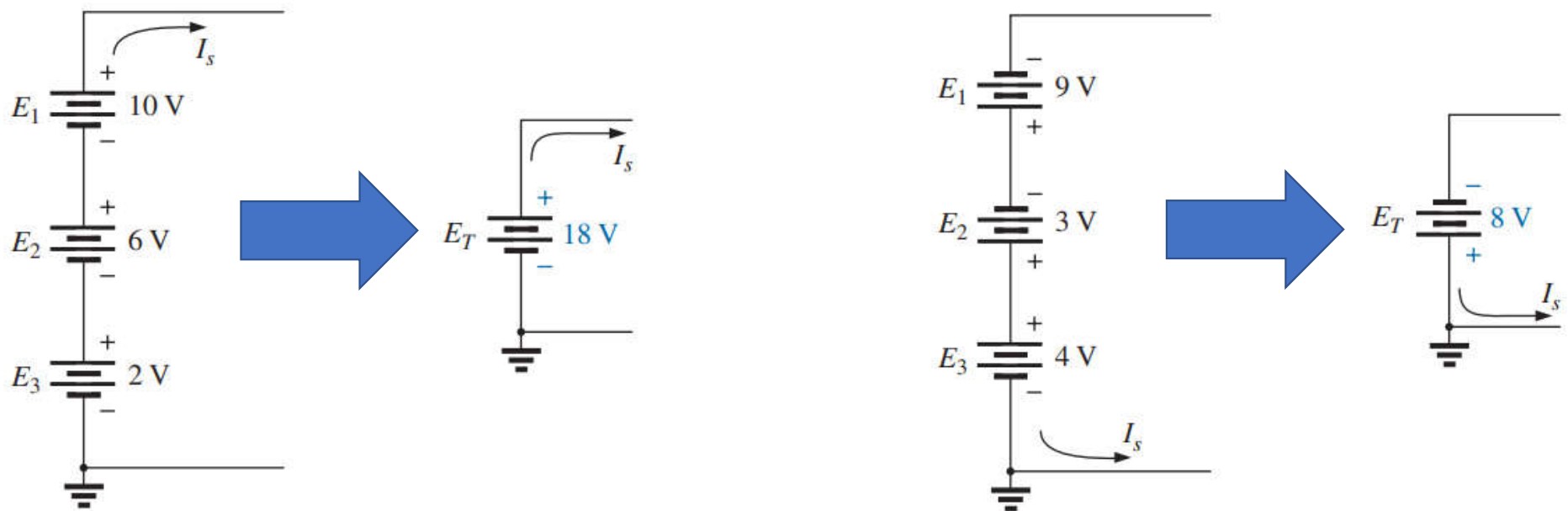


**Fig. 5.3 Reducing Series Voltage Sources to a Single Source**
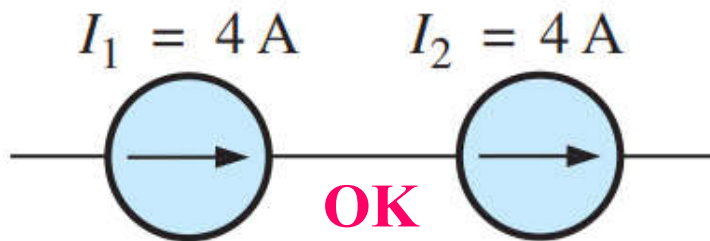
## CURRENT SOURCES IN SERIES

Current sources **to be connected in series** must have same current ratings through their voltage ratings may be same or different.



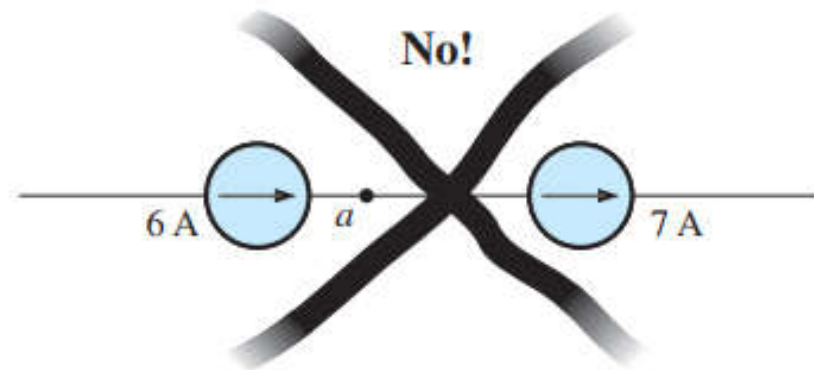Current sources of different current ratings **should not be connected in series.**



# Chapter 6

## Parallel DC Circuit



## Two Elements are in Parallel

Two **elements**, **branches**, or **circuits** are in parallel:

1. They have **two points in common**.
2. The **currents are not the same** through the two parallel elements.
3. The **voltage are the same across** the two parallel elements.

**Figure 1:**  $R_1$  and  $R_2$  are parallel since they have two common points  $a$  and  $b$ .

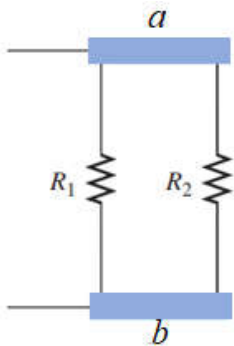


Figure 1

**Figure 2:**  $R_1$  and  $R_2$  are parallel since they have two common points  $a$  and  $b$ .  $R_3$  is series with the parallel combination of  $R_1$  and  $R_2$ .

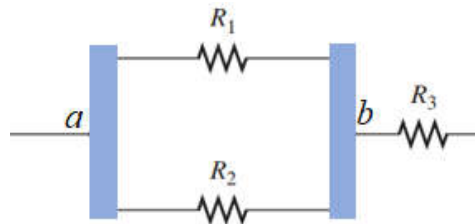


Figure 2

**Figure 3:**  $R_1$  and  $R_2$  are in series. The series combination of  $R_1$  and  $R_2$  are parallel with  $R_3$ .


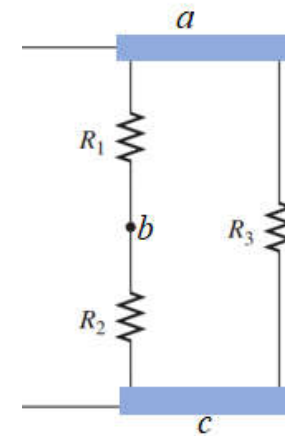


Figure 3
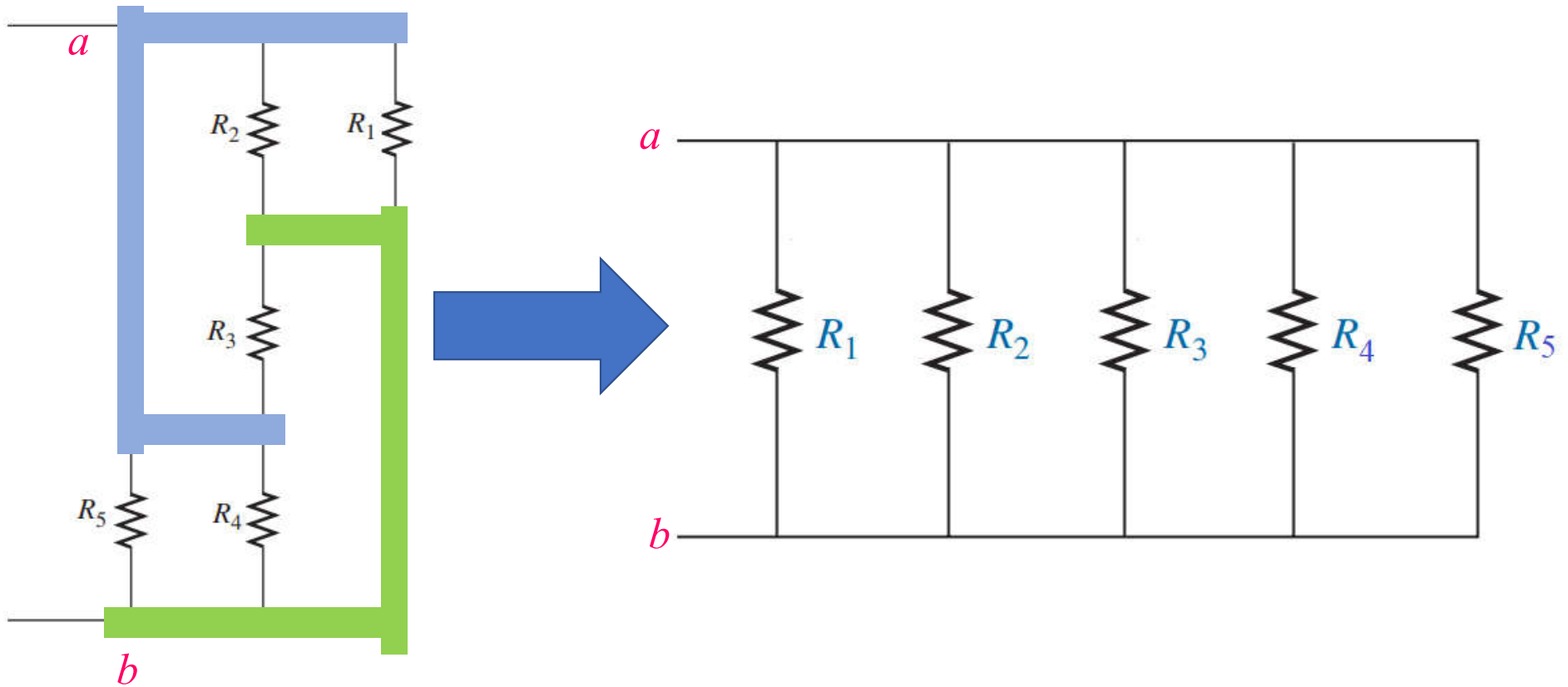
## Identify the Combination of Connection for the Following Circuit




## 6.2 Parallel Resistance

- ❖ The **total or net or effective or equivalent conductance** of a parallel configuration is **the sum of the value of individual conductance**, that is Eq. (6.2).
- ❖ The reciprocal of the total or effective or net or equivalent resistance of a parallel circuit is equal to the sum of the reciprocal of the individual resistances, that is Eq. (6.1). Eq. (6.3) can be obtained from Eq. (6.1).

$$G_T = G_1 + G_2 + G_3 + \cdots + G_N \quad (\text{siemens, S}) \quad (6.2)$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \cdots + \frac{1}{R_N} \quad (6.1)$$

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \cdots + \frac{1}{R_N}} \quad (6.3)$$

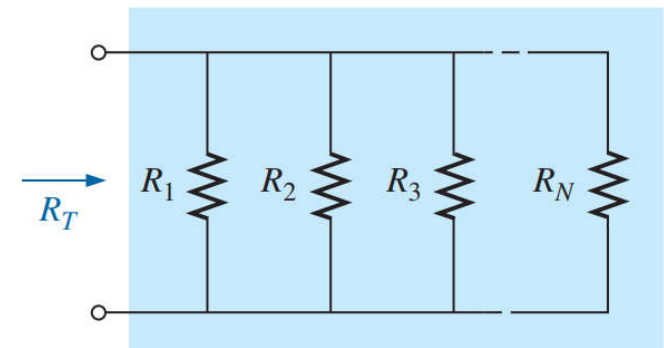

**FIG. 6.3** Parallel combination of resistors.



- ❖ The total or equivalent resistance is the smallest of all the individual resistances. that is Eq. (6.1.1).
- ❖ The total resistance of  $n$  resistors of the same value in parallel is simply *divide the value of one of the resistors by the number of resistor in parallel*; that is as Eq. (6.4)

$$R_T < R_1; R_T < R_2; \dots, R_T < R_N \quad (6.1.1)$$

$$\text{If } R_1 = R_2 = R_3 = \dots = R_N = R \quad R_T = \frac{R}{N} \quad (6.4)$$

### Special Case: Two Parallel Resistors

The total resistance of two parallel resistors is simply the product of their values divided by their sum.

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2} \quad \therefore R_T = \frac{R_1 R_2}{R_1 + R_2} \quad (6.5)$$


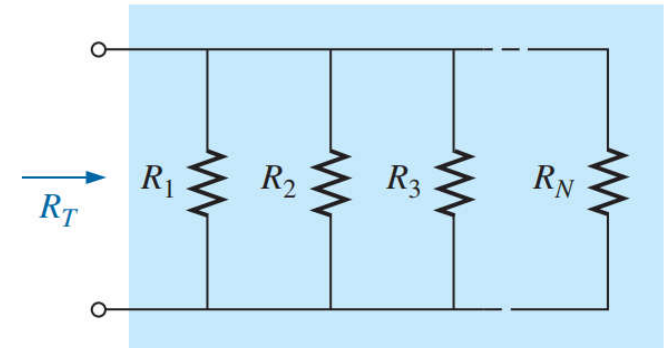


FIG. 6.3 Parallel combination of resistors.

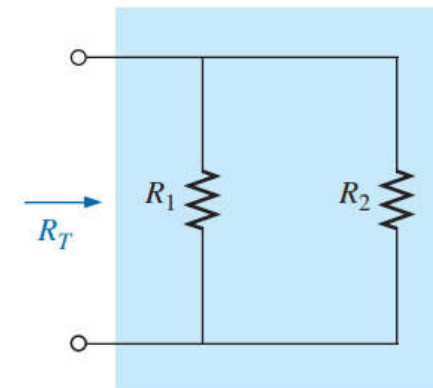

### EXAMPLE 6.1

- a.** Find the total conductance of the parallel network in Fig. 6.4.  
**b.** Find the total resistance of the same network using (i) the results of part (a), (ii) using Eq. (6.3) and (iii) using Eq. (6.5).

**Solution:** **a.**  $G_1 = \frac{1}{R_1} = \frac{1}{3\Omega} = 0.333 \text{ S}$ ,  $G_2 = \frac{1}{R_2} = \frac{1}{6\Omega} = 0.167 \text{ S}$

$$G_T = G_1 + G_2 = 0.333 \text{ S} + 0.167 \text{ S} = \mathbf{0.5 \text{ S}}$$

**b. (i)**  $R_T = \frac{1}{G_T} = \frac{1}{0.5 \text{ S}} = \mathbf{2 \Omega}$

(ii) Applying Eq. (6.3):

$$\begin{aligned} R_T &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{\frac{1}{3\Omega} + \frac{1}{6\Omega}} \\ &= \frac{1}{0.333 \text{ S} + 0.167 \text{ S}} = \frac{1}{0.5 \text{ S}} = \mathbf{2 \Omega} \end{aligned}$$

(iii) Applying Eq. (6.5):

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(3\Omega)(6\Omega)}{3\Omega + 6\Omega} = \frac{18\Omega}{9\Omega} = \mathbf{2 \Omega}$$

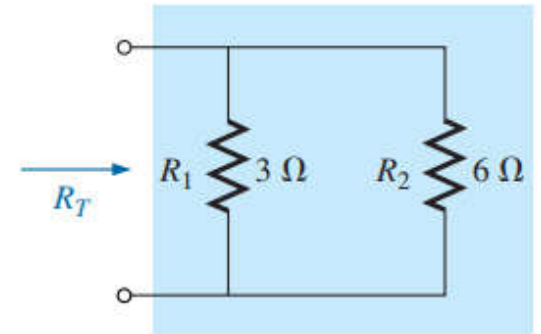


FIG. 6.4

**EXAMPLE 6.3** Find the total resistance of the configuration in Fig. 6.7.

**Solution: Method 1**

$$G_1 = \frac{1}{R_1} = \frac{1}{1\Omega} = 1.0 \text{ S}, \quad G_2 = \frac{1}{R_2} = \frac{1}{4\Omega} = 0.25 \text{ S}, \quad G_3 = \frac{1}{R_3} = \frac{1}{5\Omega} = 0.2 \text{ S}$$


$$G_T = G_1 + G_2 + G_3 = 1.0 \text{ S} + 0.25 \text{ S} + 0.2 \text{ S} = 1.45 \text{ S} \quad R_T = \frac{1}{G_T} = \frac{1}{1.45 \text{ S}} = \mathbf{0.69 \Omega}$$

**Method 2:** Applying Eq. (6.3):


$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{1\Omega} + \frac{1}{4\Omega} + \frac{1}{5\Omega}} = \frac{1}{1.0 \text{ S} + 0.25 \text{ S} + 0.2 \text{ S}} = \frac{1}{1.45 \text{ S}} \approx \mathbf{0.69 \Omega}$$

**Method 2:** Applying Eq. (6.5):  $R_{T1} = \frac{R_2 R_3}{R_2 + R_3} = \frac{(4\Omega)(5\Omega)}{4\Omega + 5\Omega} \cong 2.22 \Omega$

$$R_T = \frac{R_1 R_{T1}}{R_1 + R_{T1}} = \frac{(1\Omega)(2.22\Omega)}{1\Omega + 2.22\Omega} \cong \mathbf{0.69 \Omega}$$

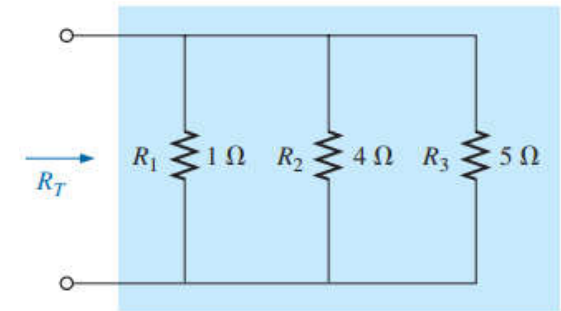


**FIG. 6.7**

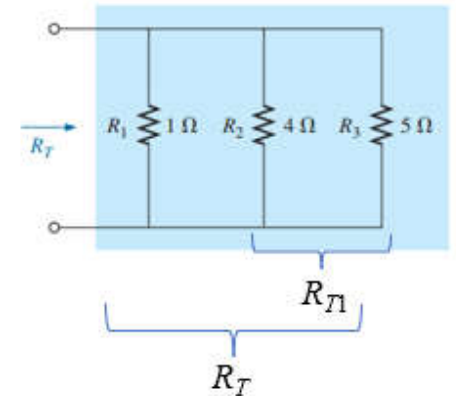

**EXAMPLE 6.5** Find the total resistance of the parallel resistors in (i) Fig. 6.9 and (ii) Fig. 6.11.

**Solution:** In both figures the individual resistance value are equal.

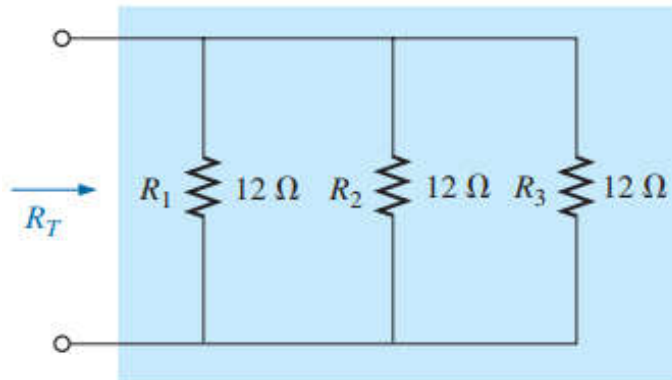


**FIG. 6.9**

**For Fig. 6.9:**

$$R_1 = R_2 = R_3 = R = 12\ \Omega$$

**Total resistance:** Applying Eq. (6.4):

$$R_T = \frac{R}{N} = \frac{12\ \Omega}{3} = 4\ \Omega$$

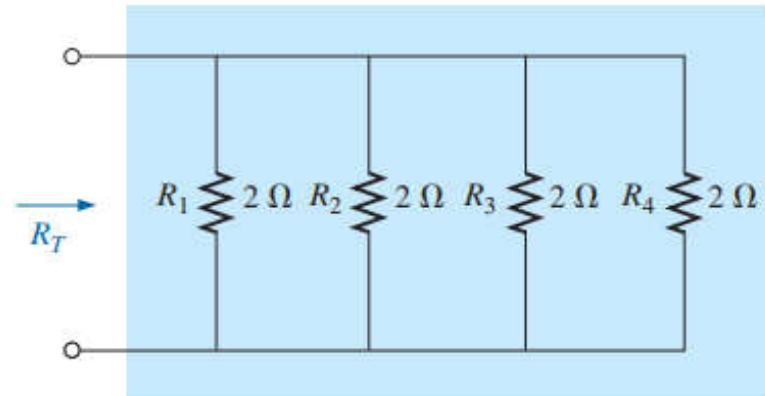

**FIG. 6.11**

**For Fig. 6.11:**

$$R_1 = R_2 = R_3 = R_4 = R = 2\ \Omega$$

**Total resistance:** Applying Eq. (6.3):

$$R_T = \frac{R}{N} = \frac{2\ \Omega}{4} = 0.5\ \Omega$$

**Problem 9 [P. 235]** Determine  $R_1$  for the network in Fig. 6.80

**Solution:** Here, all resistance are connected in parallel.

Let,  $R_2 = 24\ \Omega$ ,  $R_3 = 24\ \Omega$ , and  $R_4 = 120\ \Omega$

We know that,  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$


$$\frac{1}{R_1} = \frac{1}{R_T} - \left[ \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right]$$

$$= \frac{1}{10\ \Omega} - \left[ \frac{1}{24\ \Omega} + \frac{1}{24\ \Omega} + \frac{1}{120\ \Omega} \right]$$

$$= 0.1\ \text{S} + 0.042\ \text{S} + 0.042\ \text{S} + 0.008\ \text{S} = 0.192\ \text{S}$$

$$R_1 = \frac{1}{0.192\ \text{S}} = \mathbf{5.21\ \Omega}$$

**Practice Example 6.10 and 6.11**

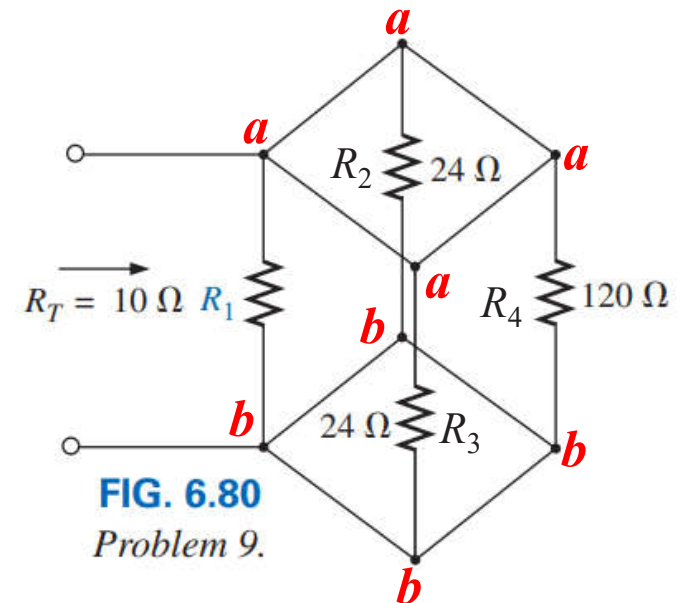

**Practice Book Problem [SECTION 6.2 Parallel Resistors] Problems: 1, 3, 4, 5, 7 and 8**

A **parallel circuit** is one in which several resistances are connected across one another in such a way that one terminal of each is connected to from a junction point while the remaining ends are also joined to form another junction point.

**Voltage in a parallel circuit:** the voltage is always the same across parallel elements.


$$V_1 = V_2 = V_3 = \dots = V_n = E \quad (6.6)$$

**Current Calculation of a Parallel circuit:**  
According ohm's law, the current of the following circuit is as follows:

$$I_s = \frac{E}{R_T} \quad (6.7)$$

$$I_1 = \frac{V_1}{R_1} = \frac{E}{R_1}; \quad I_2 = \frac{V_2}{R_2} = \frac{E}{R_2}; \quad I_n = \frac{V_n}{R_n} = \frac{E}{R_n} \quad (6.8)$$

## 6.3 Parallel Circuit

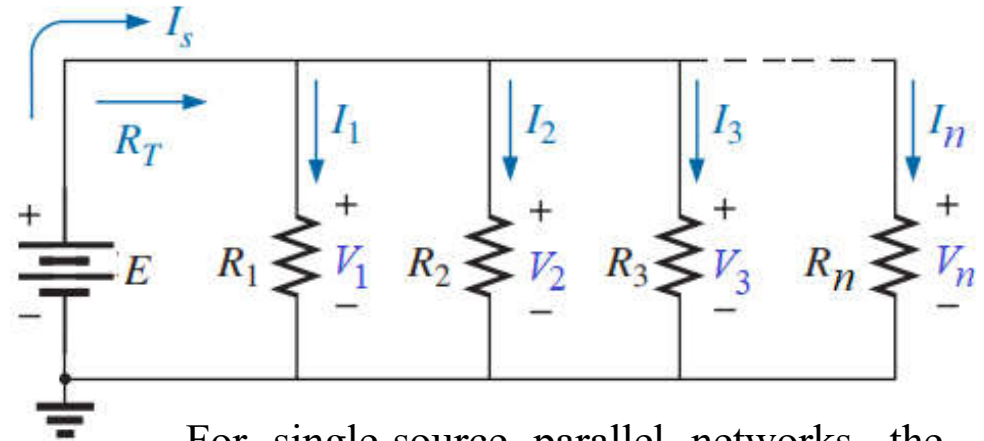

For single-source parallel networks, the source current ( $I_s$ ) is always equal to the sum of the individual branch currents.

$$I_s = I_1 + I_2 + I_3 \dots I_n \quad (6.9)$$

If  $R_1 = R_2 = R_3 = \dots = R_n = R$

$$I_1 = I_2 = I_3 = \dots = I_n = \frac{I_s}{n}$$

**EXAMPLE 6.13** For the parallel network in Fig. 6.23.

- Find the total resistance.
- Calculate the source current.
- Determine the current through each branch.


**Solution:**

- a. Applying Eq. (6.3):

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{10\ \Omega} + \frac{1}{220\ \Omega} + \frac{1}{1.2\ \text{k}\Omega}}$$
$$= \frac{1}{100 \times 10^{-3} + 4.545 \times 10^{-3} + 0.833 \times 10^{-3}} = \frac{1}{105.38 \times 10^{-3}}$$
$$R_T = \mathbf{9.49\ \Omega}$$

- b. Using Ohm's law:

$$I_s = \frac{E}{R_T} = \frac{24\ \text{V}}{9.49\ \Omega} = \mathbf{2.53\ \text{A}}$$

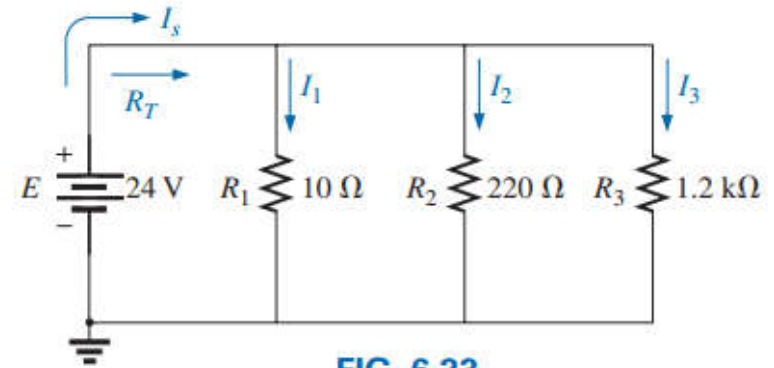

**FIG. 6.23**

*Parallel network for Example 6.13.*

- c. Applying Ohm's law:

$$I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{24\ \text{V}}{10\ \Omega} = \mathbf{2.4\ \text{A}}$$

$$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{24\ \text{V}}{220\ \Omega} = \mathbf{0.11\ \text{A}}$$

$$I_3 = \frac{V_3}{R_3} = \frac{E}{R_3} = \frac{24\ \text{V}}{1.2\ \text{k}\Omega} = \mathbf{0.02\ \text{A}}$$



**EXAMPLE 6.14** Given the information provided in Fig. 6.24.

- Determine  $R_3$ .
- Find the applied voltage  $E$ .
- Find the source current  $I_s$ .
- Find  $I_2$ .

**Solutions:**

a. Applying Eq. (6.1):  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$


Substituting:  $\frac{1}{4\ \Omega} = \frac{1}{10\ \Omega} + \frac{1}{20\ \Omega} + \frac{1}{R_3}$

so that  $0.25\ \text{S} = 0.1\ \text{S} + 0.05\ \text{S} + \frac{1}{R_3}$

and  $0.25\ \text{S} = 0.15\ \text{S} + \frac{1}{R_3}$

with  $\frac{1}{R_3} = 0.1\ \text{S}$

and  $R_3 = \frac{1}{0.1\ \text{S}} = 10\ \Omega$

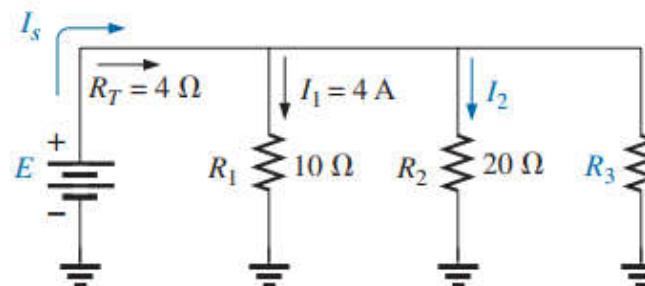

**FIG. 6.24**

*Parallel network for Example 6.14.*

b. Using Ohm's law:

$$E = V_1 = I_1 R_1 = (4\ \text{A})(10\ \Omega) = 40\ \text{V}$$

c.  $I_s = \frac{E}{R_T} = \frac{40\ \text{V}}{4\ \Omega} = 10\ \text{A}$

d. Applying Ohm's law:

$$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{40\ \text{V}}{20\ \Omega} = 2\ \text{A}$$

**Practice Book Problem [SECTION 6.3 Parallel Circuits] Problems: 10 to 17**



## 6.6 Current Division in Parallel Circuit

### Current Divider Rule (CDR)


**Current pass through individual resistance in a series circuit :** According ohm's law, the of the following circuit is as follows:

$$I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{R_T}{R_1} I_s = \frac{G_1}{G_T} I_s \quad (6.14.1)$$

$$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{R_T}{R_2} I_s = \frac{G_2}{G_T} I_s \quad (6.14.2)$$

...
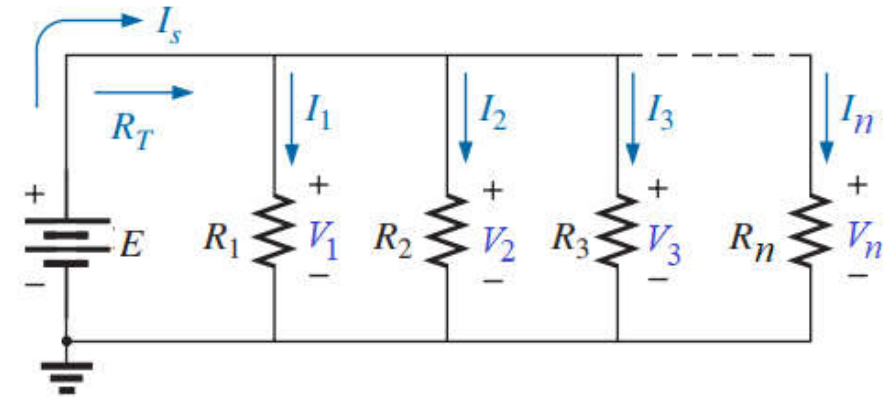
$$I_n = \frac{V_n}{R_n} = \frac{E}{R_n} = \frac{R_T}{R_n} I_s = \frac{G_n}{G_T} I_s \quad (6.14.n)$$



Based on the Eq. (6.14.1) to (6.14.n), a general equation can be written as follows:

$$I_x = \frac{R_T}{R_x} I_s = \frac{G_x}{G_T} I_s \quad (6.8)$$

**Current Divider Rule (CDR):** The current through any branch of a parallel resistive network is equal to the total resistance of the parallel network divided by the resistor of interest and multiplied by the total current entering the parallel configuration.

**EXAMPLE 6.6.1** For the following parallel network as shown in following figure. Using current divider rule, determine the current through each branch.


**Solution:**

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{10\Omega} + \frac{1}{220\Omega} + \frac{1}{1.2 \times 10^3 \Omega}$$

$$= 105.38 \times 10^{-3} \text{ S}$$

$$R_T = \frac{1}{105.38 \times 10^{-3} \text{ S}} = 9.49 \Omega$$
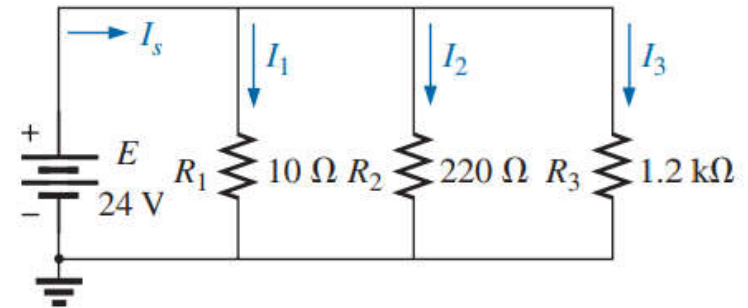
$$I_s = \frac{E}{R_T} = \frac{24 \text{ V}}{9.49 \Omega} = 2.53 \text{ A}$$



Applying current divider rule (CDR) Eq. (6.8):

$$I_1 = \frac{R_T}{R_1} I_s = \frac{9.49 \Omega}{10 \Omega} \times 2.53 \text{ A} = \mathbf{2.4 \text{ A}}$$

$$I_2 = \frac{R_T}{R_2} I_s = \frac{9.49 \Omega}{220 \Omega} \times 2.53 \text{ A} = \mathbf{0.11 \text{ A}}$$

$$I_3 = \frac{R_T}{R_3} I_s = \frac{9.49 \Omega}{1.2 \times 10^3 \Omega} \times 2.53 \text{ A} = \mathbf{0.02 \text{ A}}$$



**EXAMPLE 6.6.2** For the following parallel network as shown in following figure. Using current divider rule, determine the current through each branch.

**Solution:**


$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{10\Omega} + \frac{1}{20\Omega} + \frac{1}{10\Omega}} = 4\Omega$$

Applying current divider rule CDR) Eq. (6.8):

$$I_1 = \frac{R_T}{R_1} I_s = \frac{4\Omega}{10\Omega} \times 10\text{ A} = 4\text{ A}$$

$$I_2 = \frac{R_T}{R_2} I_s = \frac{4\Omega}{20\Omega} \times 10\text{ A} = 2\text{ A}$$
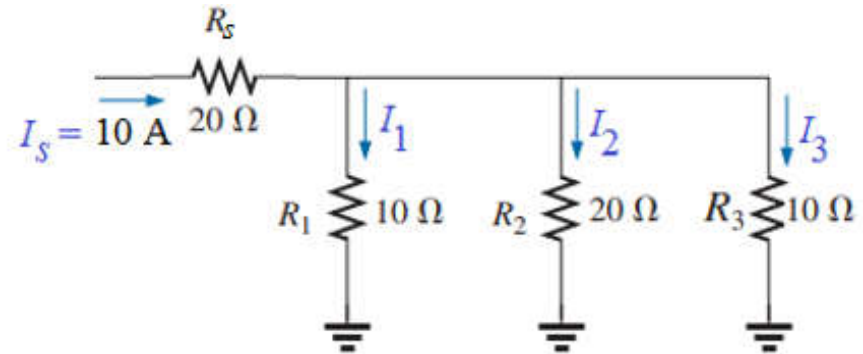
$$I_3 = \frac{R_T}{R_3} I_s = \frac{4\Omega}{10\Omega} \times 10\text{ A} = 4\text{ A}$$



Since  $R_1$  and  $R_3$  are equal, the current  $I_1$  and  $I_3$  must be equal.

Since  $R_2$  is twice  $R_1$  or  $R_3$ , the current  $I_2$  must be one-half  $I_1$  or  $I_3$ .

**Practice Book Problem [SECTION 6.6 CDR] Problems: 29 to 34**



## 6.5 KIRCHHOFF'S CURRENT LAW (KCL)

### Statement:

(1) The algebraic sum of the currents entering and leaving a junction (or region) of a network is zero.

$$\sum I_{\text{entering}} - \sum I_{\text{leaving}} = 0 \quad (6.13.1)$$

(2) The sum of the currents entering a junction (or region) of a network must equal the sum of the currents leaving the same junction (or region).

$$\sum I_{\text{entering}} = \sum I_{\text{leaving}} \quad (6.13)$$

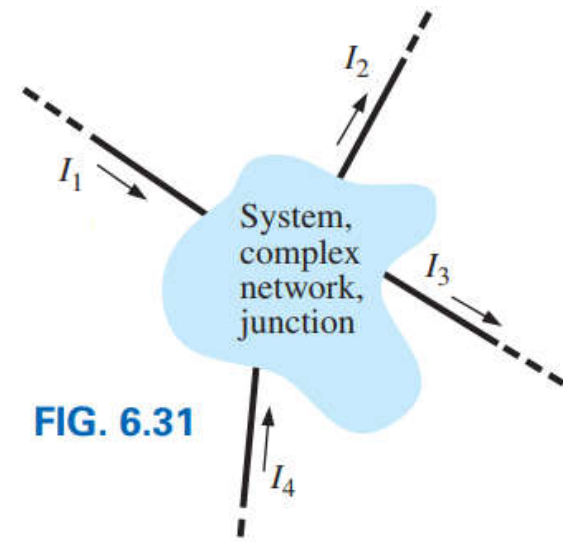


FIG. 6.31

$$I_1 + I_4 - I_2 - I_3 = 0$$

$$I_1 + I_4 = I_2 + I_3$$

**EXAMPLE 6.17** Determine currents  $I_1$ ,  $I_3$ ,  $I_4$ , and  $I_5$  for the network in Fig. 6.34.

**Solution:** At node  $a$ :


$$\begin{aligned}\sum I_i &= \sum I_o \\ I &= I_1 + I_2 \\ 5 \text{ A} &= I_1 + 4 \text{ A} \\ \text{and} \quad I_1 &= 5 \text{ A} - 4 \text{ A} = 1 \text{ A}\end{aligned}$$

At node  $b$ :

$$\begin{aligned}\sum I_i &= \sum I_o \\ I_1 &= I_3 \\ \text{and} \quad I_3 &= I_1 = 1 \text{ A}\end{aligned}$$

At node  $c$ :

$$\begin{aligned}\sum I_i &= \sum I_o \\ I_2 &= I_4 \\ \text{and} \quad I_4 &= I_2 = 4 \text{ A}\end{aligned}$$

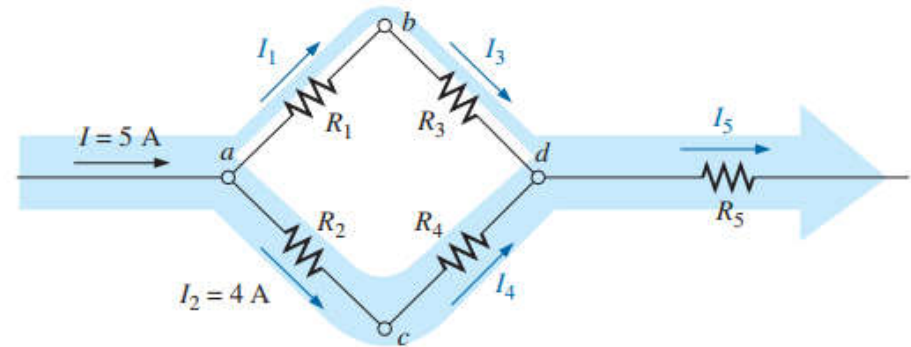

**FIG. 6.34**

Four-node configuration for Example 6.17.

At node  $d$ :

$$\begin{aligned}\sum I_i &= \sum I_o \\ I_3 + I_4 &= I_5 \\ 1 \text{ A} + 4 \text{ A} &= I_5 = 5 \text{ A}\end{aligned}$$

### EXAMPLE 6.21

- Determine currents  $I_1$  and  $I_3$  for the network in Fig. 6.40.
- Find the source current  $I_s$ .

#### Solutions:

- Since  $R_1$  is twice  $R_2$ , the current  $I_1$  must be one-half  $I_2$ , and

$$I_1 = \frac{I_2}{2} = \frac{2 \text{ mA}}{2} = \mathbf{1 \text{ mA}}$$

Since  $R_2$  is three times  $R_3$ , the current  $I_3$  must be three times  $I_2$ , and


$$I_3 = 3I_2 = 3(2 \text{ mA}) = \mathbf{6 \text{ mA}}$$

- Applying Kirchhoff's current law:

$$\sum I_i = \sum I_o$$

$$I_s = I_1 + I_2 + I_3$$

$$I_s = 1 \text{ mA} + 2 \text{ mA} + 6 \text{ mA} = \mathbf{9 \text{ mA}}$$

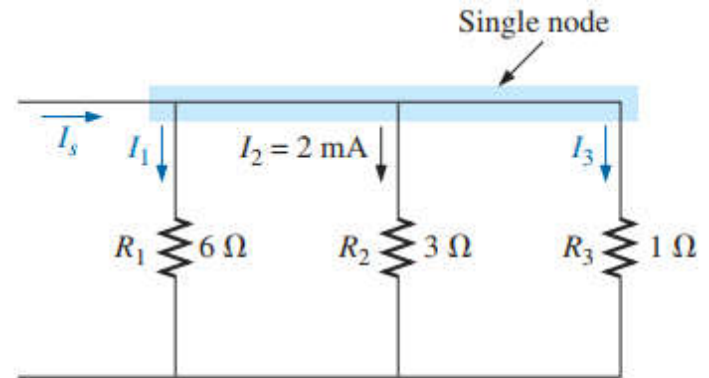

**FIG. 6.40**

*Parallel network for Example 6.21.*



**Problem 25 [P. 238]** Using Kirchoff's current law, find the unknown currents for the complex configurations in Fig. 6.95(b).

**Solution:** Consider four ( $a$ ,  $b$ ,  $c$ , and  $d$ ) nodes are here.

**At node  $a$ :** 6 A is entering and 2 A is leaving so consider  $I_1$  is leaving.

According to KCL at node  $a$ , we have:  $6 \text{ A} = I_1 + 2 \text{ A} = 9 \text{ A}$

$$\therefore I_1 = 6 \text{ A} - 2 \text{ A} = 4 \text{ A}$$

**At node  $b$ :**  $I_1 = 4 \text{ A}$  and 5 A are entering so consider  $I_2$  is leaving.


According to KCL at node  $b$ , we have:  $I_2 = 4 \text{ A} + 5 \text{ A} = 9 \text{ A}$

**At node  $c$ :**  $I_2 = 9 \text{ A}$  current is entering and 3 A is leaving so consider  $I_3$  is leaving.

According to KCL at node  $c$ , we have:  $9 \text{ A} = I_3 + 3 \text{ A} \quad \therefore I_3 = 9 \text{ A} - 3 \text{ A} = 6 \text{ A}$

**At node  $d$ :** 3 A and 10 A are entering so consider  $I_4$  is leaving.

According to KCL at node  $d$ , we have:  $I_4 = 3 \text{ A} + 10 \text{ A} = 13 \text{ A}$

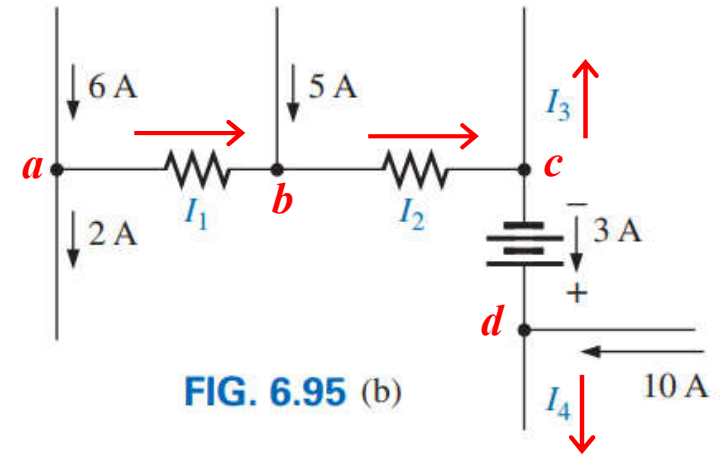

**FIG. 6.95 (b)**

## Practice Book Problem [SECTION 6.5 KCL] Problems: 24 to 28



## 6.4 Power Distribution in a Parallel Circuit

In any electrical system, the power supplied or applied or delivered will equal the power dissipated or absorbed or consumed.

$$P_E = P_{R1} + P_{R2} + P_{R3} \quad (6.10)$$

$$P_E = EI_s \text{ (watt, W)} \quad (6.11)$$

$$P_{R1} = V_1 I_1 = I_1^2 R_1 = \frac{V_1^2}{R_1}$$

$$P_{R2} = V_2 I_2 = I_2^2 R_2 = \frac{V_2^2}{R_2}$$

$$P_{R3} = V_3 I_3 = I_3^2 R_3 = \frac{V_3^2}{R_3}$$

(watt, W) (6.12)


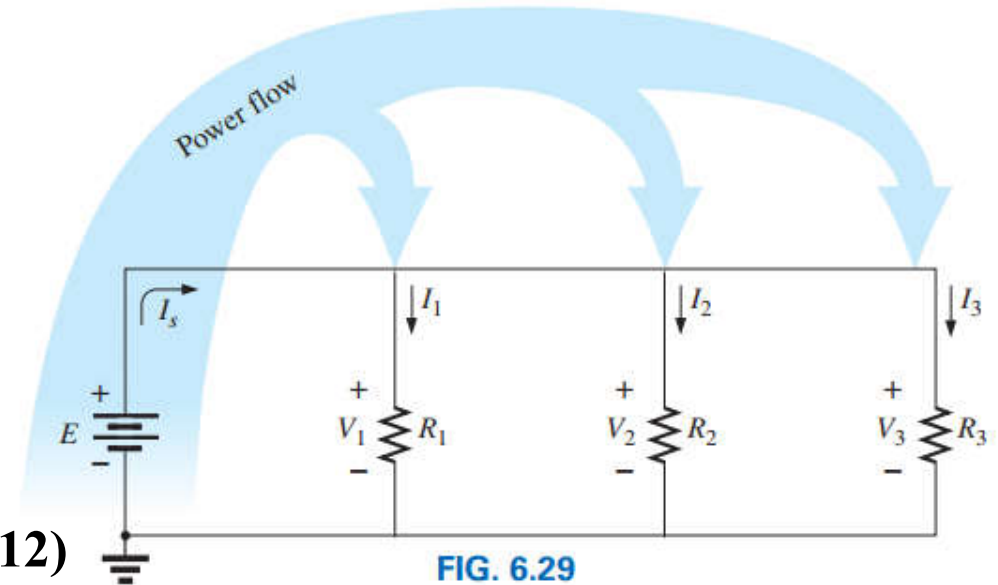


FIG. 6.29

Power flow in a dc parallel network.

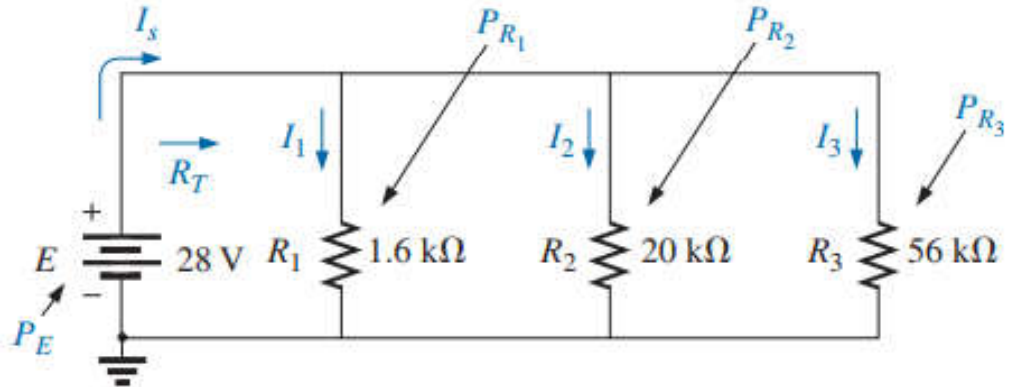**EXAMPLE 6.15** For the parallel network in Fig. 6.30:

- Determine the total resistance  $R_T$ .
- Find the source current ( $I_s$ ) and the current ( $I_1$ ,  $I_2$ , and  $I_3$ ) through each resistor.
- Verify KCL.
- Calculate the power delivered by the source.
- Determine the power absorbed by each parallel resistor.
- Verify Eq. (6.10)



**Solution:** (a) 
$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{1.6 \times 10^3 \Omega} + \frac{1}{20 \times 10^3 \Omega} + \frac{1}{56 \times 10^3 \Omega}}$$
$$= \frac{1}{625 \times 10^{-6} \text{ S} + 50 \times 10^{-6} \text{ S} + 17.867 \times 10^{-6} \text{ S}} = \frac{1}{692.867 \times 10^{-6} \text{ S}} = 1.44 \text{ k}\Omega$$

**b.** Find the source current ( $I_s$ ) and the current ( $I_1$ ,  $I_2$ , and  $I_3$ ) through each resistor.

$$R_T = 1.44 \text{ k}\Omega$$


**(b)** Applying Ohm's Law :

$$I_s = \frac{E}{R_T} = \frac{28 \text{ V}}{1.44 \times 10^3 \Omega} = \mathbf{19.4 \text{ mA}}$$

$$I_1 = \frac{R_T}{R_1} I_s = \frac{E}{R_1} = \frac{26 \text{ V}}{1.6 \times 10^3 \Omega} = \mathbf{17.5 \text{ A}}$$

$$I_2 = \frac{R_T}{R_2} I_s = \frac{E}{R_2} = \frac{26 \text{ V}}{20 \times 10^3 \Omega} = \mathbf{1.4 \text{ A}}$$
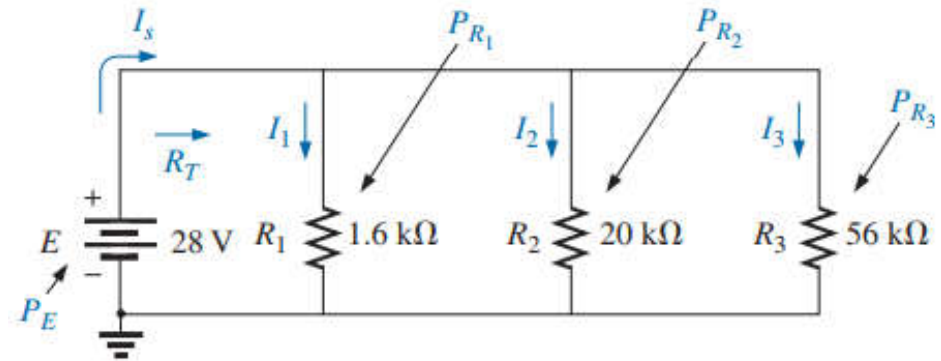
$$I_3 = \frac{R_T}{R_3} I_s = \frac{E}{R_3} = \frac{26 \text{ V}}{56 \times 10^3 \Omega} = \mathbf{0.5 \text{ A}}$$



**(c)** According to KCL :  $I_s = I_1 + I_2 + I_3$

$$\mathbf{19.4 \text{ mA} = 17.5 \text{ mA} + 1.4 \text{ mA} + 0.5 \text{ mA} = 19.4 \text{ mA}}$$

- d. Calculate the power delivered by the source.  
 e. Determine the power absorbed by each parallel resistor.  
 f. Verify Eq. (6.10)

**Solution:**  $R_T = 1.44 \text{ k}\Omega$      $I_s = 19.44 \text{ mA}$

$$I_1 = 17.5 \text{ A}; I_2 = 1.4 \text{ A}; I_3 = 0.5 \text{ A}$$

d. Applying Eq. (6.11):  $P_E = EI_s = (28 \text{ V})(19.4 \text{ mA}) = 543.2 \text{ mW}$

e. Applying each form of the power equation:


$$P_1 = V_1 I_1 = EI_1 = (28 \text{ V})(17.5 \text{ mA}) = 490 \text{ mW}$$

$$P_2 = I_2^2 R_2 = (1.4 \text{ mA})^2 (20 \text{ k}\Omega) = 39.2 \text{ mW}$$

$$P_3 = \frac{V_3^2}{R_3} = \frac{E^2}{R_3} = \frac{(28 \text{ V})^2}{56 \text{ k}\Omega} = 14 \text{ mW}$$

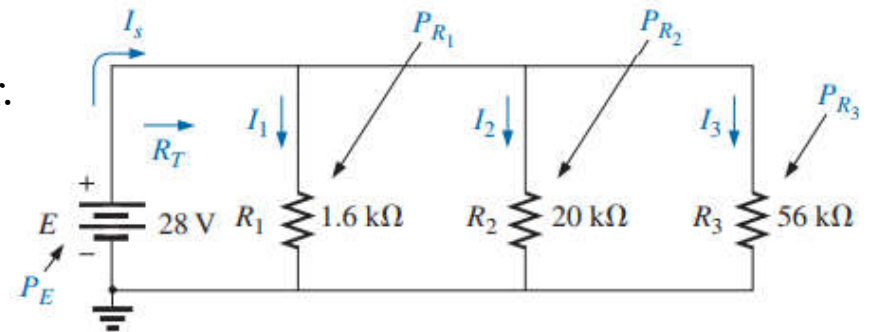f.  $P_E = P_{R_1} + P_{R_2} + P_{R_3}$

$$543.2 \text{ mW} = 490 \text{ mW} + 39.2 \text{ mW} + 14 \text{ mW} = 543.2 \text{ mW} \quad (\text{checks})$$



**Practice Book Problem**  
**[SECTION 6.4 Power**  
**Distribution]**

**Problems: 19 to 23**

## 6.7 VOLTAGE SOURCES IN PARALLEL

Voltage sources can be placed in parallel only if:

- (i) They have the same voltage rating.
- (ii) Positive terminal should be connected with positive terminal and Negative terminal should be connected with negative terminal

**Voltage sources to be connected in parallel must have same voltage rating through their current rating may be same or different.**

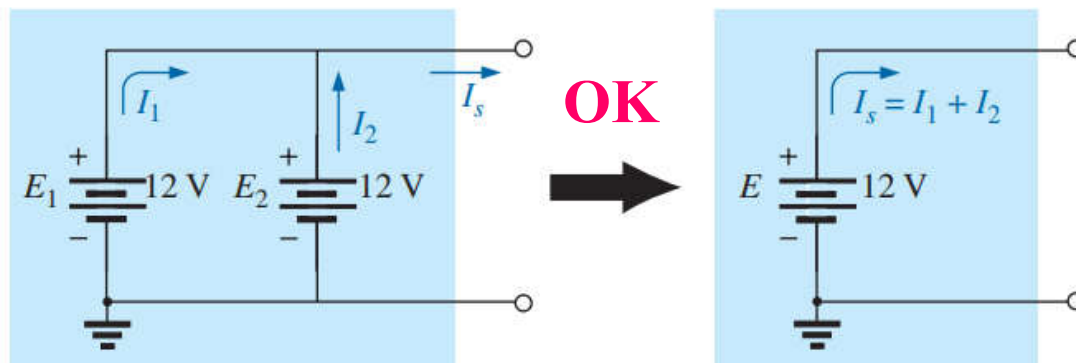


FIG. 6.47

*Demonstrating the effect of placing two ideal supplies of the same voltage in parallel.*

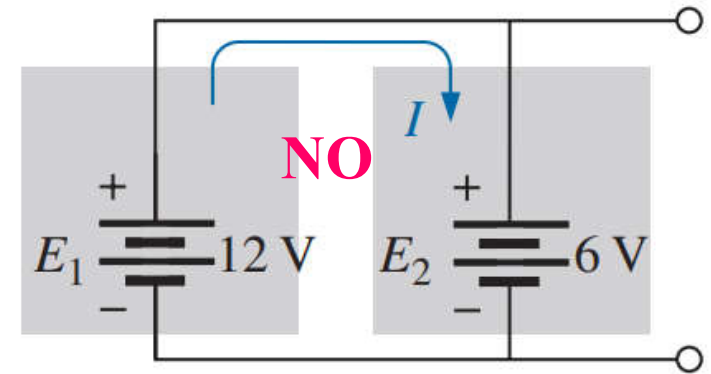



FIG. 6.48

**Should not be connected**
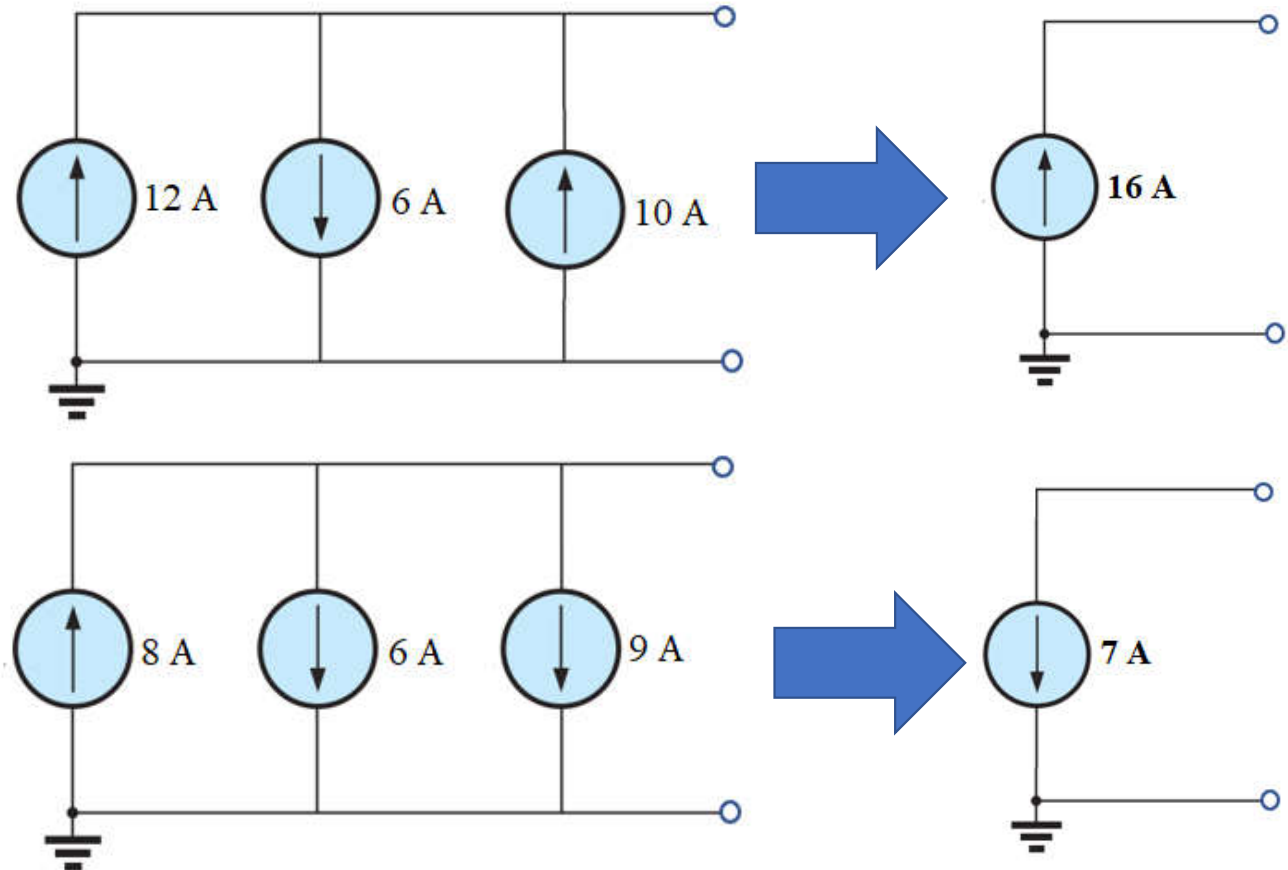
## CURRENT SOURCES IN PARALLEL

Current sources of different current ratings are not connected in series.

The current sources to be connected in parallel must have same voltage rating through their current ratings may be same or different.



**Reducing Parallel Current Sources to a Single Source**


**Problem 22 [P. 238]** A portion of a residential service to a home is depicted in Fig. 6.92.

a. Determine the current through each parallel branch of the system.

b. Calculate the current drawn from the 120 V source. Will the 20 A breaker trip?

c. What is the total resistance of the network?

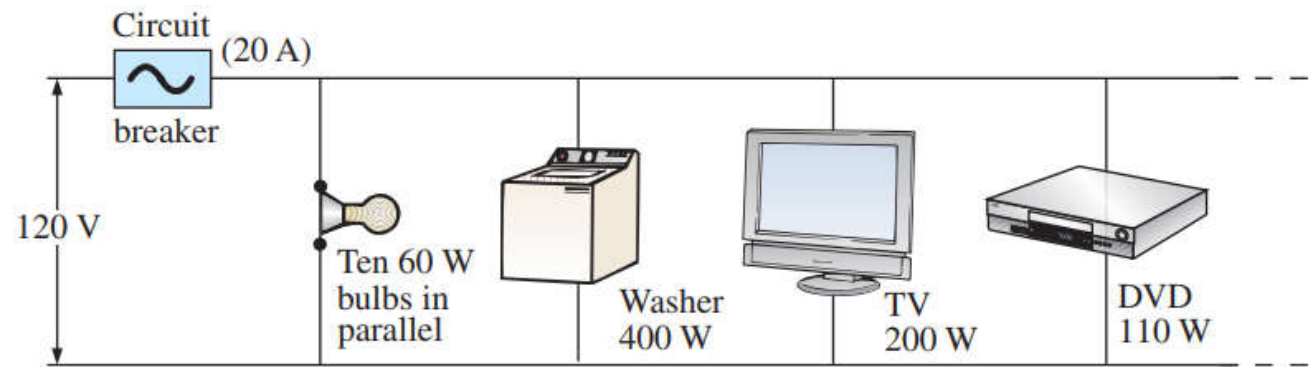d. Determine the power delivered by the source. How does it compare to the sum of the wattage ratings appearing in Fig. 6.92?



**Solution:** a. We know that:  $P = VI \quad \therefore I = \frac{P}{V}$

$$\text{For bulbs: } I_b = \frac{10 \times 60 \text{ W}}{120 \text{ V}} = 5 \text{ A}$$

$$\text{For washer: } I_w = \frac{400 \text{ W}}{120 \text{ V}} = 3.33 \text{ A}$$

$$\text{For TV: } I_{tv} = \frac{200 \text{ W}}{120 \text{ V}} = 1.667 \text{ A}$$


$$\text{For DVD: } I_{dvd} = \frac{110 \text{ W}}{120 \text{ V}} = 0.917 \text{ A}$$



- b. Calculate the current drawn from the 120 V source. Will the 20 A breaker trip?
- c. What is the total resistance of the network?
- d. Determine the power delivered by the source. How does it compare to the sum of the wattage ratings appearing in Fig. 6.92?

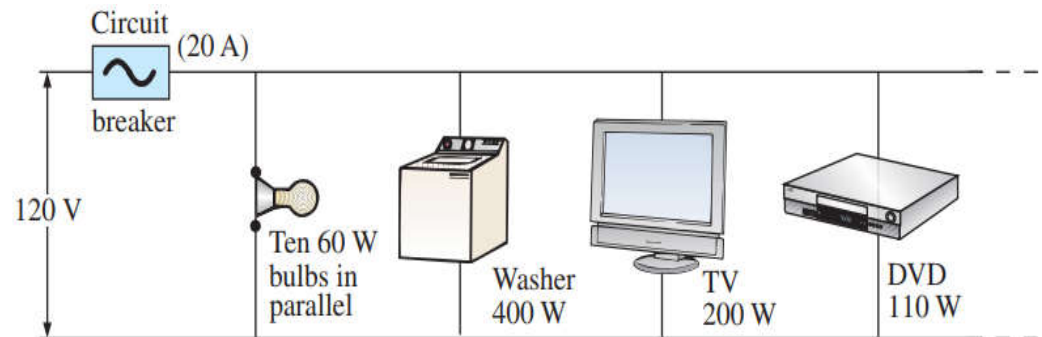b. Applying KCL we have:

$$\begin{aligned}
 I_s &= I_b + I_w + I_{tv} + I_{dvd} \\
 &= 5 \text{ A} + 3.333 \text{ A} + 1.667 \text{ A} + 0.917 \text{ A} \\
 &= 10.917 \text{ A}
 \end{aligned}$$



Since source current less than 20 circuit breaker will not trip.

c.  $R_T = \frac{E}{I_s} = \frac{120 \text{ V}}{10.917 \text{ A}} = 10.99 \text{ } \Omega$

d.  $P_E = EI_s = (120 \text{ V})(10.917 \text{ A}) = 1310 \text{ W}$

$$P_w = (10 \times 60) \text{ W} + 400 \text{ W} + 200 \text{ W} + 110 \text{ W} = 1310 \text{ W}$$

Power delivered by the source ( $P_E$ ) is **equal** to the sum of the wattage ratings ( $P_w$ ).




# OPEN CIRCUITS SHORT CIRCUITS


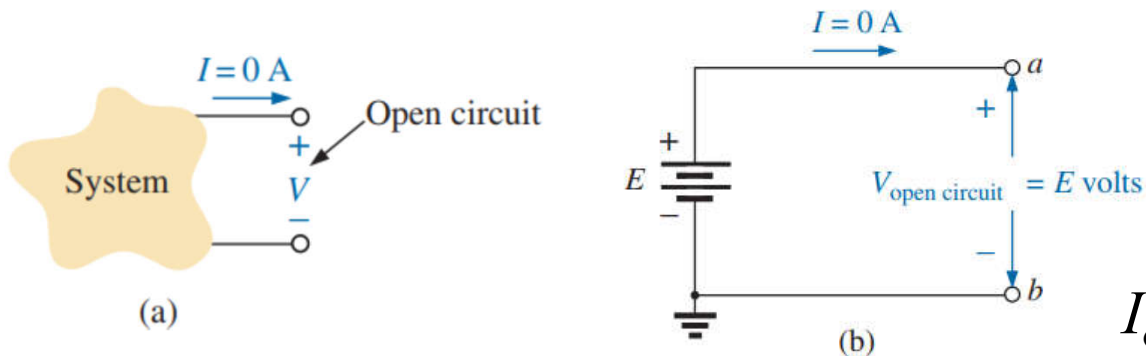
## 6.8 OPEN CIRCUITS

An **open circuit** is two isolated terminals not connected by any kind of element.





An open circuit can have a potential difference (voltage) across its terminals, but the current is always zero (0) amperes.

$$I_{oc} = 0 \text{ A}$$


$$R_{oc} = \infty \text{ (Infinite)}$$

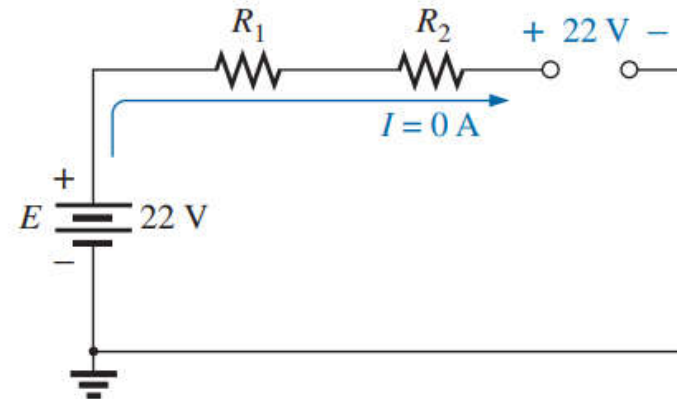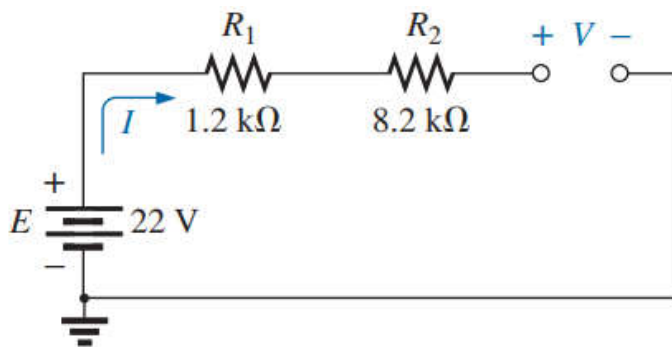**EXAMPLE 6.27.1** Determine the unknown voltage ( $V$ ) and current ( $I$ ) for the following network.


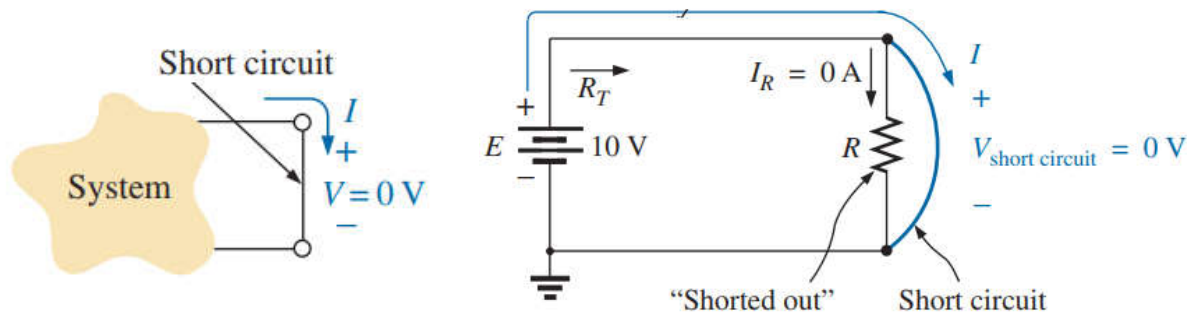
## 6.8 Short CIRCUITS

A **short circuit** is a very low resistance, direct connection between two terminals of a network.





A short circuit can carry a current of a level determined by the external circuit, but the potential difference (voltage) across its terminals is always zero (0) volts.


$$V_{sc} = 0 \text{ V}$$

$$R_{sc} = 0 \text{ (Zero)}$$

**EXAMPLE 6.27.2** Determine the unknown voltage ( $V$ ) and current ( $I$ ) for the following network.

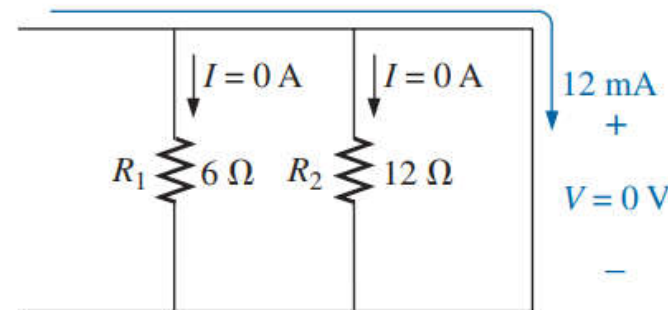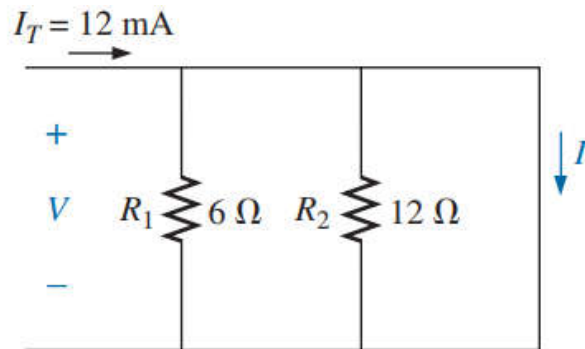

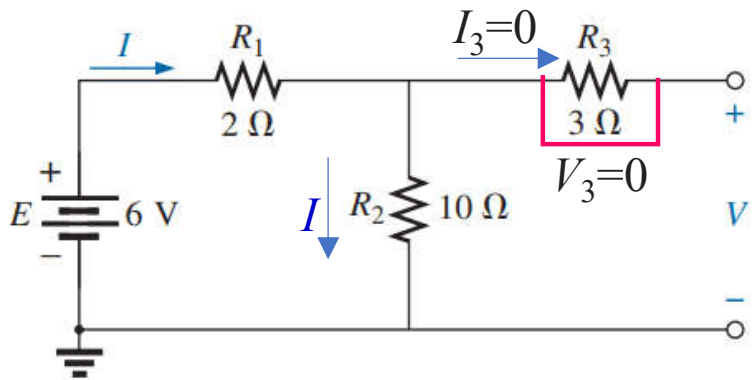**EXAMPLE 6.28.1** Determine the unknown voltage ( $V$ ) and current ( $I$ ) for the following network.




Due to the open circuit, the current flow ( $I_3$ ) through the  $R_3$  is zero. Thus, the current  $I$  flows through  $R_1$  and  $R_2$  and  $V$  is equal to the voltage drop across the resistance  $R_2$ .

$$V = \frac{R_2}{R_1 + R_2} E = \frac{10 \Omega}{2 \Omega + 10 \Omega} \times 6 \text{ V} = \mathbf{5 \text{ V}}$$

$$I = \frac{E}{R_1 + R_2} = \frac{6 \text{ V}}{2 \Omega + 10 \Omega} = \mathbf{0.5 \text{ A}}$$

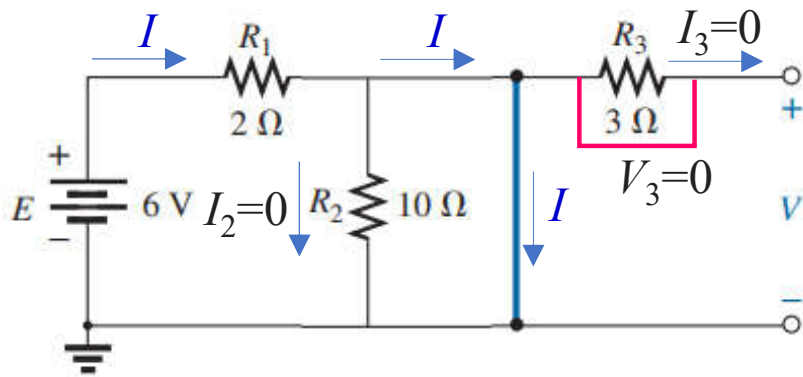**EXAMPLE 6.28.2** Determine the unknown voltage ( $V$ ) and current ( $I$ ) for the following network.




Due to the open circuit, the current flow ( $I_3$ ) through the  $R_3$  is zero and since  $R_2$  is shorted the current flow ( $I_2$ ) through the  $R_2$  is zero. Thus, the current  $I$  flows through  $R_1$  and short circuit and  $V = \mathbf{0 \text{ V}}$ .

$$I = \frac{E}{R_1} = \frac{6 \text{ V}}{2 \Omega} = \mathbf{3 \text{ A}}$$


**Problem 38 [Ch 6]** A For the network in Fig. 6.108:

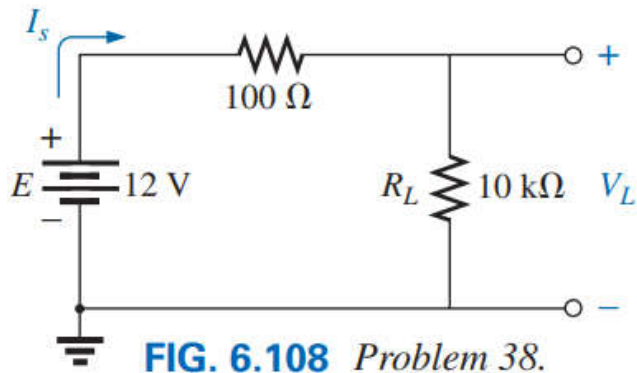- (a) Determine  $I_s$  and  $V_L$ .
- (b) Determine  $I_s$  if  $R_L$  is shorted out.
- (c) Determine  $V_L$  if  $R_L$  is replaced by an open circuit.




$$(a) \quad I_s = \frac{12 \text{ V}}{100 \Omega + 1 \text{ k}\Omega} = \mathbf{10.91 \text{ mA}}$$
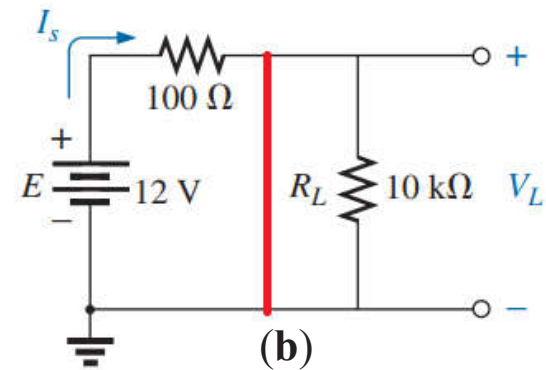
$$V_L = I_s R_L = (10.91 \times 10^{-3}) \times (1 \times 10^3) = \mathbf{10.91 \text{ V}}$$



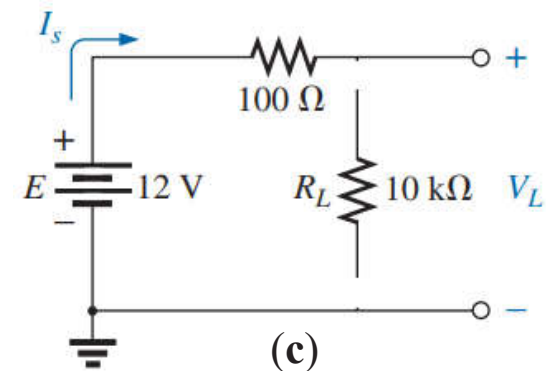
$$(b) \quad I_s = \frac{12 \text{ V}}{100 \Omega} = \mathbf{120 \text{ mA}}$$




$$(c) \quad V_L = E = \mathbf{12 \text{ V}}$$

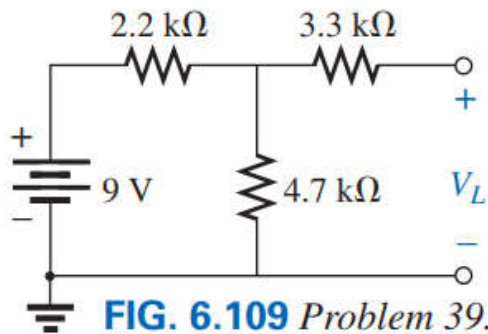**Problem 39 [Ch 6]** For the network in Fig. 6.109:


- Determine the open-circuit voltage  $V_L$ .
- If the  $2.2\text{ k}\Omega$  resistor is short circuited, what is the new value of  $V_L$ ?
- Determine  $V_L$  if the  $4.7\text{ k}\Omega$  resistor is replaced by an open circuit.


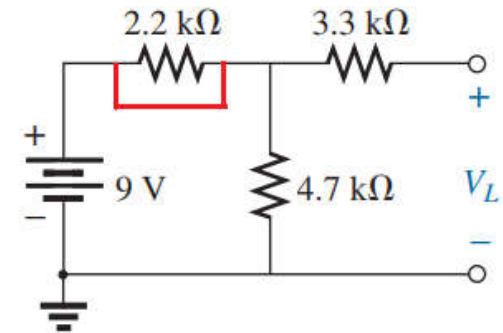
$$(a) \quad V_L = \frac{(4.7\text{ k}\Omega) \times (9\text{ V})}{2.2\text{ k}\Omega + 4.7\text{ k}\Omega} = \mathbf{6.13\text{ V}}$$


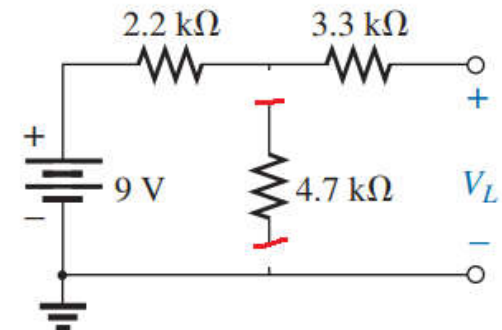
$$(b) \quad V_L = E = \mathbf{9\text{ V}}$$




$$(c) \quad V_L = E = \mathbf{9\text{ V}}$$

# Chapter 7

## Series-Parallel DC Circuit



## 7.3 REDUCE AND RETURN APPROACH

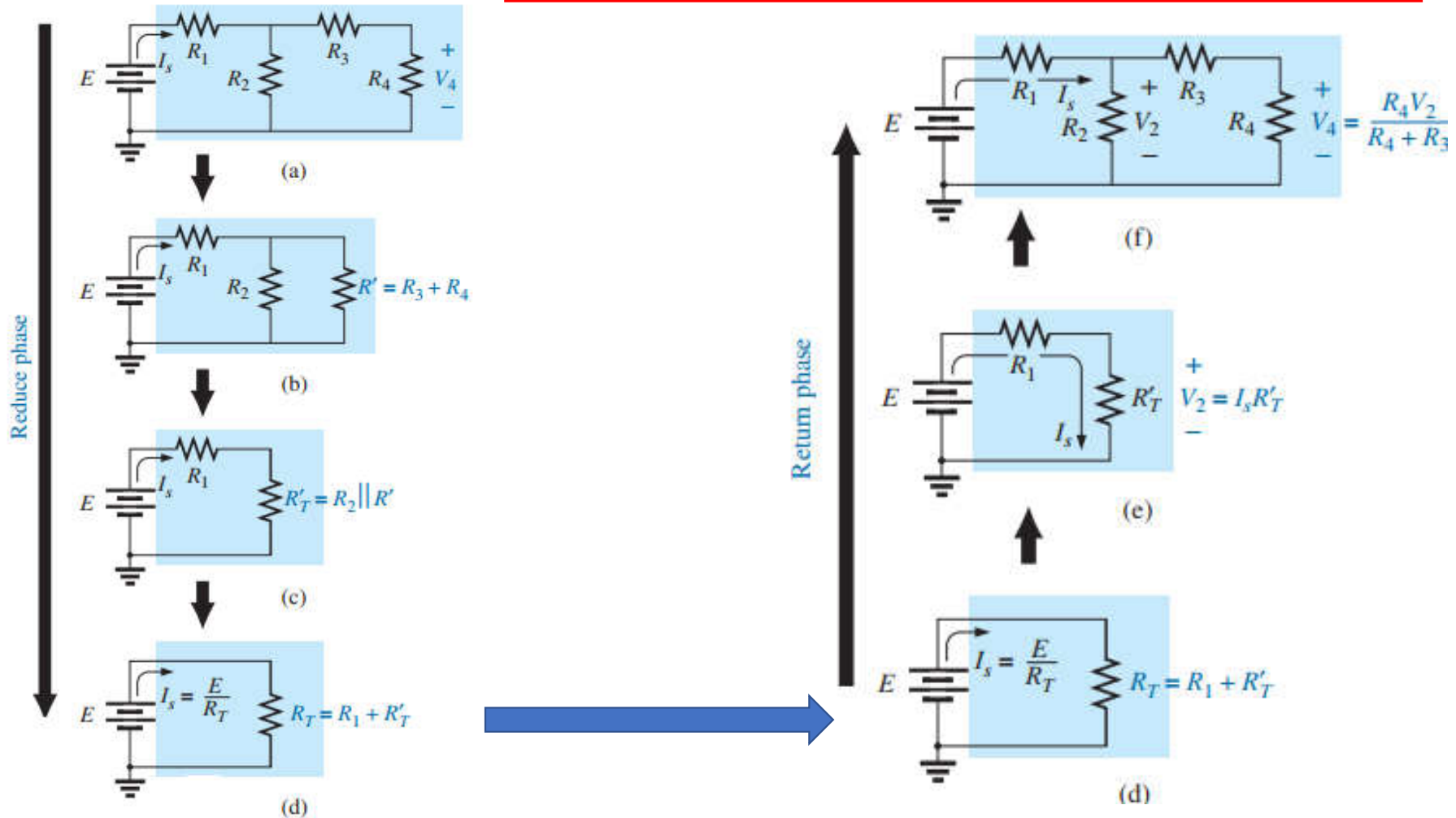



**EXAMPLE 7.1** Find current  $I_3$  for the series-parallel network in Fig. 7.3.

**Solution:** Checking for series and parallel elements, we find that resistors  $R_2$  and  $R_3$  are in parallel. Their total resistance is:

$$R_4 = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3} = \frac{(12 \text{ k}\Omega)(6 \text{ k}\Omega)}{12 \text{ k}\Omega + 6 \text{ k}\Omega} = 4 \text{ k}\Omega$$

Redraw the circuit showing the calculated resistance  $R_4$ .

Now, resistors  $R_1$  and  $R_4$  are in series, resulting in a total resistance of


$$R_T = R_1 + R_4 = 2 \text{ k}\Omega + 4 \text{ k}\Omega = 6 \text{ k}\Omega$$

The source current is then determined using Ohm's law:


$$I_s = \frac{E}{R_T} = \frac{54 \text{ V}}{6 \text{ k}\Omega} = 9 \text{ mA}$$

Returning to Fig. 7.3, we find the current  $I_3$  as follows:

$$I_3 = \frac{R_4}{R_3} I_1 = \left( \frac{R_2}{R_2 + R_3} \right) I_1 = \left( \frac{12 \text{ k}\Omega}{12 \text{ k}\Omega + 6 \text{ k}\Omega} \right) 9 \text{ mA} = 6 \text{ mA}$$

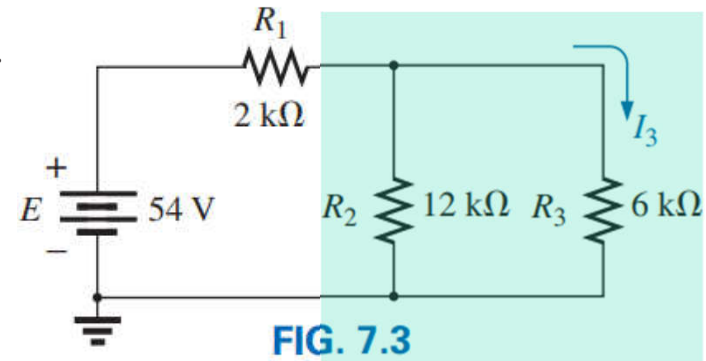

**FIG. 7.3**

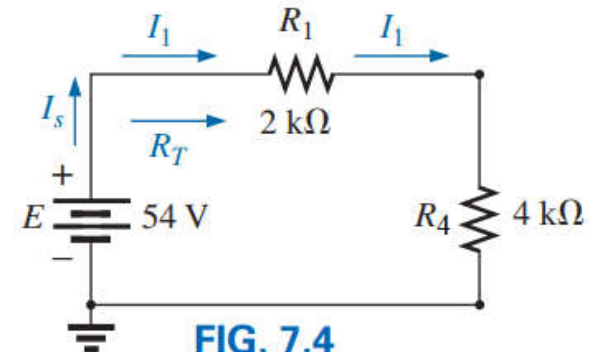

**FIG. 7.4**

**EXAMPLE 7.2** For the network in Fig. 7.5:

- Determine currents  $I_4$  and  $I_s$  and voltage  $V_2$ .
- Insert the meters to measure current  $I_4$  and voltage  $V_2$ .

**Solution:**



$$R_5 = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3} = \frac{(18 \text{ k}\Omega)(2 \text{ k}\Omega)}{18 \text{ k}\Omega + 2 \text{ k}\Omega} = 1.8 \text{ k}\Omega$$

$$I_4 = \frac{V_4}{R_4} = \frac{E}{R_4} = \frac{12 \text{ V}}{8.2 \text{ k}\Omega} = \mathbf{1.46 \text{ mA}}$$

$$V_2 = \left( \frac{R_5}{R' + R_1} \right) E = \left( \frac{1.8 \text{ k}\Omega}{1.8 \text{ k}\Omega + 6.8 \text{ k}\Omega} \right) 12 \text{ V} = \mathbf{2.51 \text{ V}}$$

$$I_1 = \frac{E}{R_1 + R_5} = \frac{12 \text{ V}}{6.8 \text{ k}\Omega + 1.8 \text{ k}\Omega} = 1.40 \text{ mA}$$

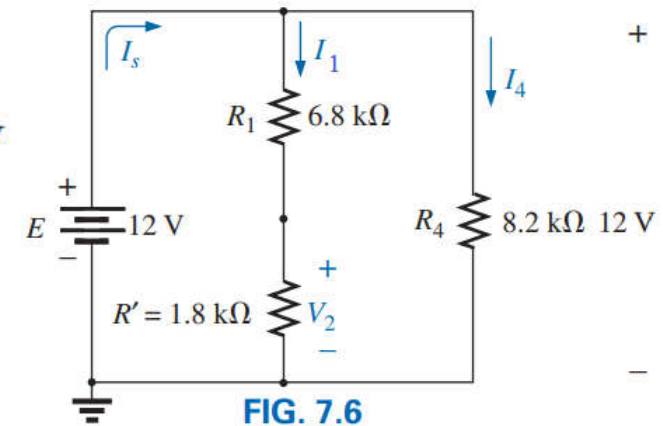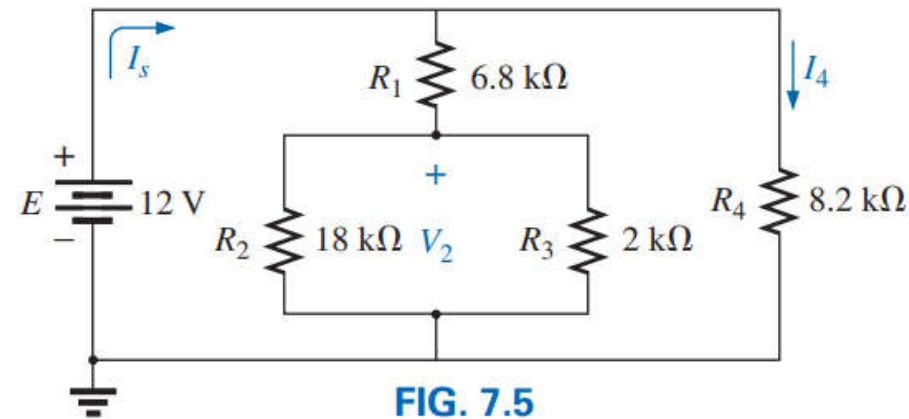and  $I_s = I_1 + I_4 = 1.40 \text{ mA} + 1.46 \text{ mA} = \mathbf{2.86 \text{ mA}}$



**Practice Book Problem [SECTIONS 7.2–7.5 Series Parallel Networks] Problems: 1 ~ 24**

## 7.4 BLOCK DIAGRAM APPROACH



**EXAMPLE 7.4** Determine all the currents and voltages for the series-parallel network in Fig. 7.12.

**Solution:**

$$R_A = \frac{R_1 R_2}{R_1 + R_2} = \frac{(9\ \Omega) \times (6\ \Omega)}{9\ \Omega + 6\ \Omega} = 3.6\ \Omega$$


$$R_B = R_3 + \frac{R_4 R_5}{R_4 + R_5} = 4\ \Omega + \frac{(3\ \Omega) \times (3\ \Omega)}{6\ \Omega + 3\ \Omega} = 4\ \Omega + 2\ \Omega = 6\ \Omega$$

$$R_C = R_6 = 3\ \Omega$$

$$R_{B//C} = \frac{R_B R_C}{R_B + R_C} = \frac{(6\ \Omega) \times (3\ \Omega)}{6\ \Omega + 3\ \Omega} = 2\ \Omega$$

$$R_T = R_A + R_{B//C} = 3.6\ \Omega + 2\ \Omega = 5.6\ \Omega$$
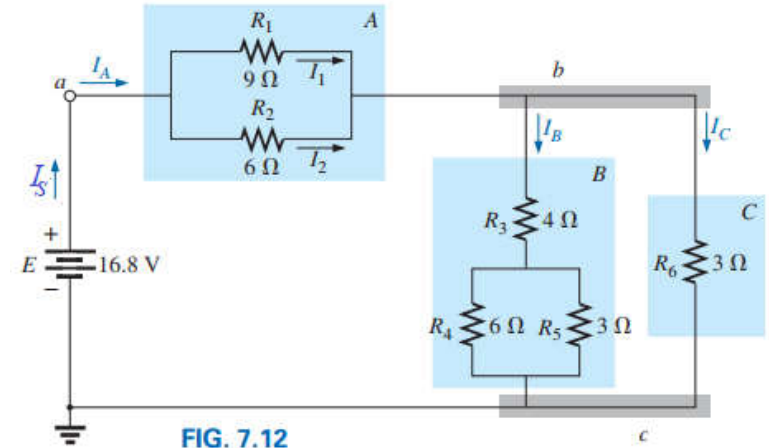
$$I_s = I_A = \frac{E}{R_T} = \frac{16.8\ \text{V}}{5.6\ \Omega} = 3\ \text{A}$$



$$I_1 = \frac{R_A}{R_1} I_s = \frac{R_2}{R_1 + R_2} I_s = \frac{6\ \Omega}{9\ \Omega + 6\ \Omega} \times 3\ \text{A} = 1.2\ \text{A}$$

$$I_2 = \frac{R_A}{R_2} I_s = \frac{R_1}{R_1 + R_2} I_s = I_s - I_1 = 3\ \text{A} - 1.2\ \text{A} = 1.8\ \text{A}$$

$$I_B = \frac{R_{B//C}}{R_B} I_s = \frac{R_C}{R_B + R_C} I_s = \frac{3\ \Omega}{6\ \Omega + 3\ \Omega} \times 3\ \text{A} = 1\ \text{A}$$

$$I_C = \frac{R_{B//C}}{R_C} I_s = \frac{R_B}{R_B + R_C} I_s = I_s - I_B = 3\ \text{A} - 1\ \text{A} = 2\ \text{A}$$

### EXAMPLE 7.7

- a. Find the voltages  $V_1$ ,  $V_3$ , and  $V_{ab}$  for the network in Fig. 7.20.  
b. Calculate the source current  $I_s$ .

#### Solution:

$$V_1 = \frac{R_1 E}{R_1 + R_2} = \frac{(5\ \Omega)(12\ \text{V})}{5\ \Omega + 3\ \Omega} = \frac{60\ \text{V}}{8} = 7.5\ \text{V}$$

$$V_3 = \frac{R_3 E}{R_3 + R_4} = \frac{(6\ \Omega)(12\ \text{V})}{6\ \Omega + 2\ \Omega} = \frac{72\ \text{V}}{8} = 9\ \text{V}$$

$$+V_1 - V_3 + V_{ab} = 0$$



$$\text{and } V_{ab} = V_3 - V_1 = 9\ \text{V} - 7.5\ \text{V} = 1.5\ \text{V}$$

b. By Ohm's law,  $I_1 = \frac{V_1}{R_1} = \frac{7.5\ \text{V}}{5\ \Omega} = 1.5\ \text{A}$



$$I_3 = \frac{V_3}{R_3} = \frac{9\ \text{V}}{6\ \Omega} = 1.5\ \text{A}$$

Applying Kirchhoff's current law,

$$I_s = I_1 + I_3 = 1.5\ \text{A} + 1.5\ \text{A} = 3\ \text{A}$$

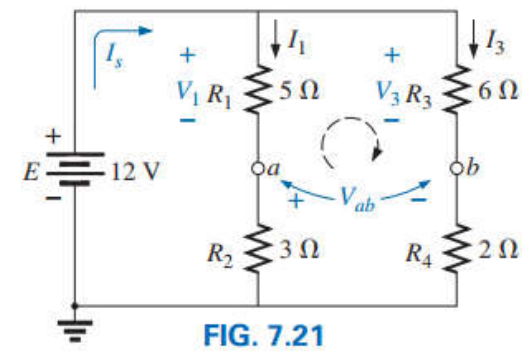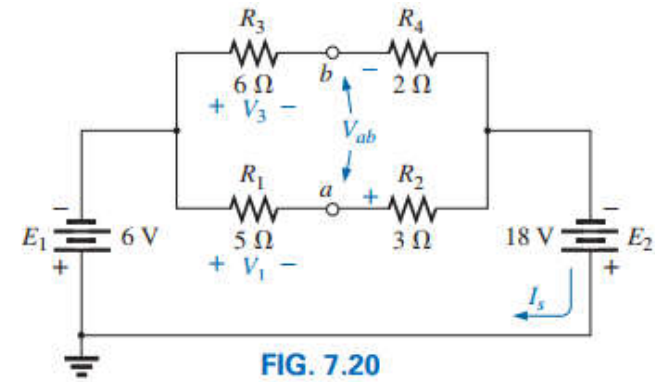

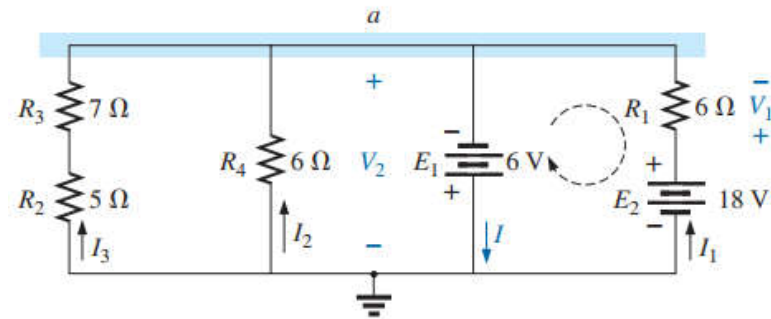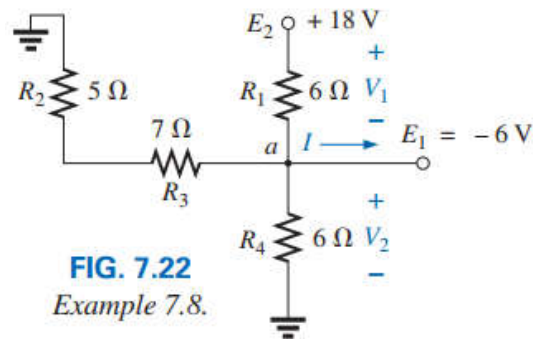**EXAMPLE 7.8** For the network in Fig. 7.22, determine the voltages  $V_1$  and  $V_2$  and the current  $I$ .



**Solution:**

Applying Kirchhoff's voltage law:

$$V_2 = -E_1 = -6 \text{ V}$$

Applying Kirchhoff's voltage law:

$$-E_1 + V_1 - E_2 = 0$$

$$\text{and } V_1 = E_2 + E_1 = 18 \text{ V} + 6 \text{ V} = 24 \text{ V}$$

Applying Kirchhoff's current law to node  $a$  yields

$$\begin{aligned} I &= I_1 + I_2 + I_3 \\ &= \frac{V_1}{R_1} + \frac{E_1}{R_4} + \frac{E_1}{R_2 + R_3} \\ &= \frac{24 \text{ V}}{6 \Omega} + \frac{6 \text{ V}}{6 \Omega} + \frac{6 \text{ V}}{12 \Omega} \\ &= 4 \text{ A} + 1 \text{ A} + 0.5 \text{ A} \\ I &= 5.5 \text{ A} \end{aligned}$$

### Problem 10:

- Find the magnitude and direction for current  $I$ ,  $I_1$ ,  $I_2$ , and  $I_3$ , for the network in Fig. 7.70.
- Indicate their direction on Fig. 7.70.

**Solution:** Voltage drop across the resistance  $R_1$  equal to 24 V. So:

$$I_1 = \frac{24 \text{ V}}{4 \Omega} = 6 \text{ A}$$

Voltage drop across the resistance  $R_3$  equal to 8 V. So:  $I_3 = \frac{8 \text{ V}}{10 \Omega} = 0.8 \text{ A}$

Voltage drop across the resistance  $R_2$  equal to the difference of 24 V and -8 V. So:

$$I_2 = \frac{24 \text{ V} - (-8 \text{ V})}{2 \Omega} = \frac{32 \text{ V}}{2 \Omega} = 16 \text{ A}$$

According to KCL:  $I = I_1 + I_2 = 6 \text{ A} + 16 \text{ A} = 22 \text{ A}$

**Practice Book Problem [SECTIONS 7.2–7.5 Series Parallel Networks] Problems: 1 ~ 24**


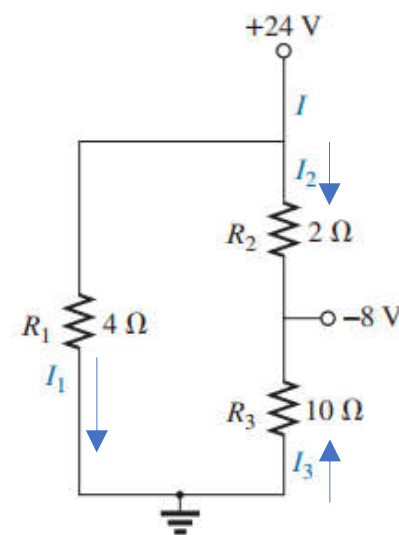


FIG. 7.70 Problem 10.

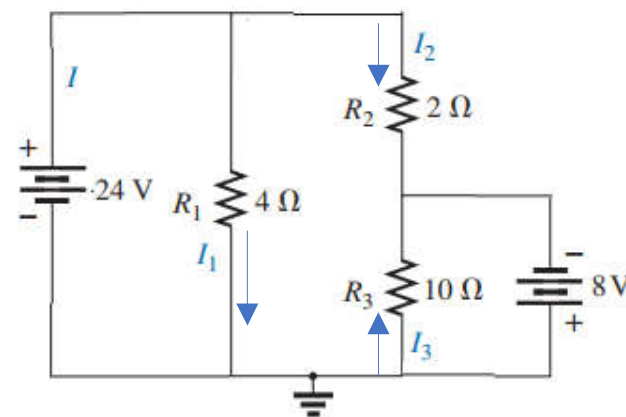



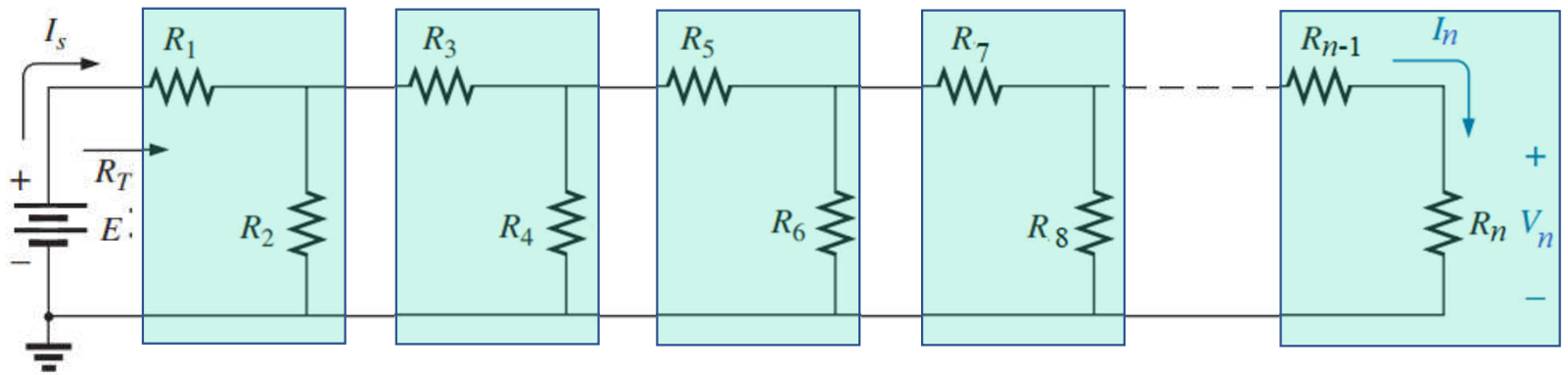
## 7.6 LADDER NETWORKS





A  **$n$ -section ladder network** appears in the following Figure.


The reason for the terminology is quite obvious for the repetitive structure.



Basically, **two approaches** are used to solve networks of this type.



- (1) Calculate the total resistance and resulting source current, and then work back through the ladder until the desired current or voltage is obtained [**Reduce and Return Approach**].
- (2) Assign a letter symbol to the last branch current ( $I_n$ ) and voltage ( $V_n$ ) and work back through the network to the source, maintaining this assigned current or other current of interest. The desired current can then be found directly.

**EXAMPLE FIG. 7.3** Determine the unknown currents  $I_s$ ,  $I_2$ ,  $I_3$ ,  $I_4$ , and  $I_6$  and voltage ( $V_6$ ) for the following network.

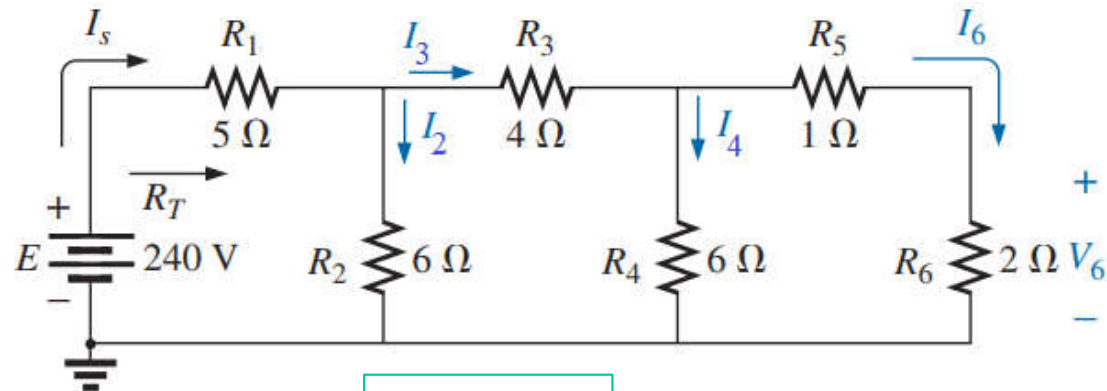


**Method 1**


$$R_7 = R_5 + R_6 = 3 \Omega$$

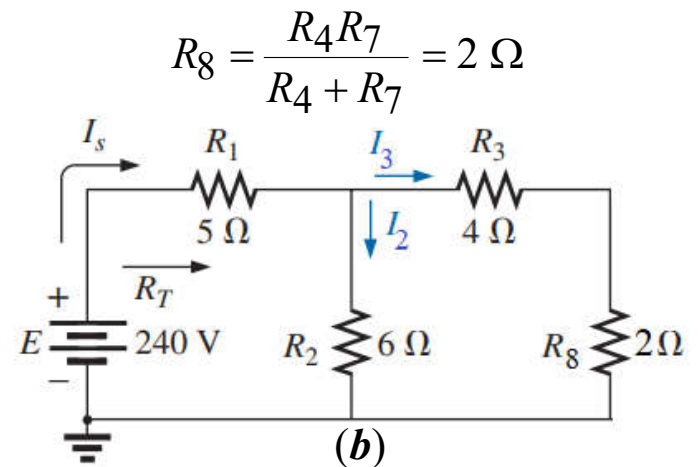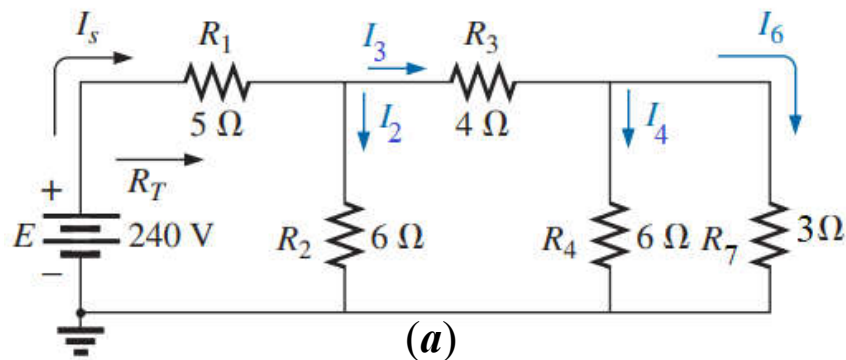


$$R_9 = R_3 + R_8 = 6 \Omega$$

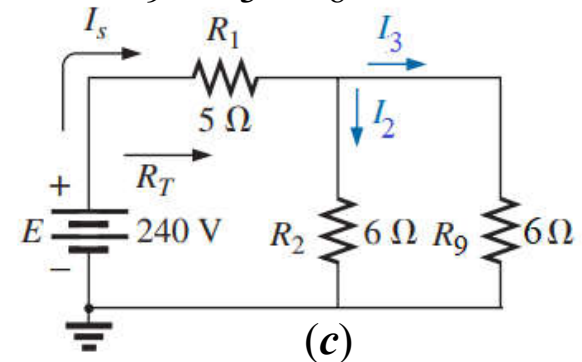
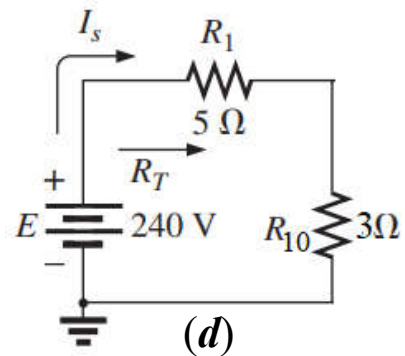
$$R_{10} = \frac{R_2 R_9}{R_2 + R_9} = 3 \Omega$$



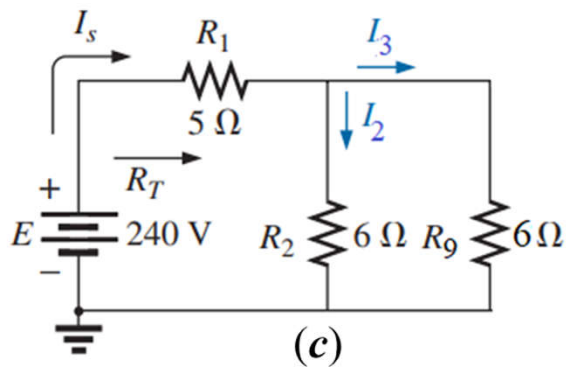
$$I_s = \frac{E}{R_1 + R_{10}} = \frac{240 \text{ V}}{5 \Omega + 3 \Omega} = 30 \text{ A}$$



From Fig. (c), we have:
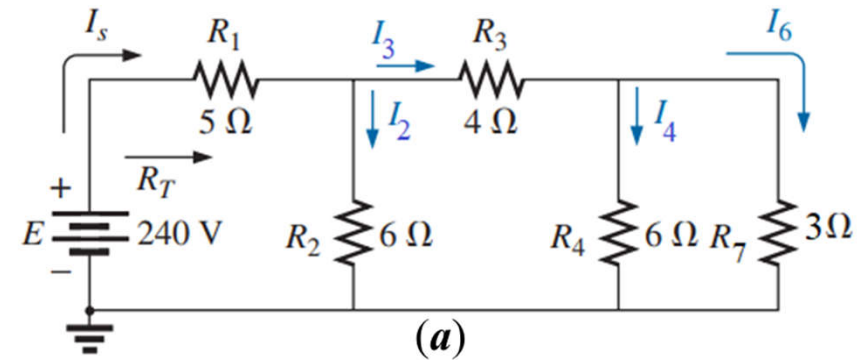
$$I_2 = I_3 = \frac{I_s}{2} = 15 \text{ A}$$




From Fig. (a), we have:

$$I_4 = \frac{R_7}{R_4 + R_7} I_3 = 5 \text{ A}$$

$$I_6 = \frac{R_4}{R_4 + R_7} I_3 = 10 \text{ A}$$

$$V_6 = I_6 R_6 = 10 \text{ A} \times 2 \Omega = \mathbf{20 \text{ V}}$$

## Method 2

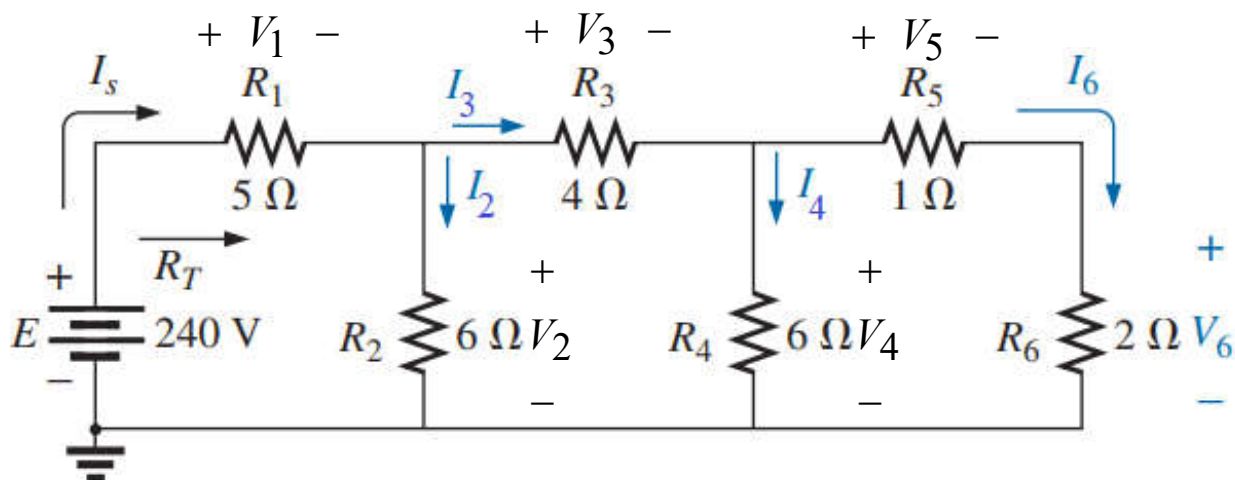

The assigned notation for the current through the final branch is  $I_6$ :

$$I_6 = \frac{V_5 + V_6}{R_5 + R_6} = \frac{V_4}{R_5 + R_6} = \frac{V_4}{3\Omega} \quad \therefore V_4 = (3\Omega)I_6$$

$$I_4 = \frac{V_4}{R_4} = \frac{V_4}{6\Omega} = \frac{(3\Omega)I_6}{6\Omega} = 0.5I_6$$

$$I_3 = I_4 + I_6 = 0.5I_6 + I_6 = 1.5I_6$$

$$V_3 = I_3 R_3 = (1.5I_6)(4\Omega) = (6\Omega)I_6$$

**Practice Problem**  
**[SECTIONS 7.6]**  
**Problems: 25 ~ 28**

$$V_2 = V_3 + V_4 = (6\Omega)I_6 + (3\Omega)I_6 = (9\Omega)I_6$$

$$I_2 = \frac{V_2}{R_2} = \frac{(9\Omega)I_6}{6\Omega} = 1.5I_6$$

$$I_s = I_2 + I_3 = 1.5I_6 + 1.5I_6 = 3I_6$$

$$V_1 = I_s R_1 = 3I_6(5\Omega) = (15\Omega)I_6$$

$$E = V_1 + V_2 = (15\Omega)I_6 + (9\Omega)I_6 = (24\Omega)I_6$$

$$I_6 = \frac{E}{24\Omega} = \frac{240\text{ V}}{24\Omega} = \mathbf{10\text{ A}}$$

$$V_6 = I_6 R_6 = 10\text{ A} \times 2\Omega = \mathbf{20\text{ V}}$$

$$I_4 = 0.5I_6 = 0.5 \times 10\text{ A} = \mathbf{5\text{ A}}$$

$$I_3 = 1.5I_6 = 1.5 \times 10\text{ A} = \mathbf{15\text{ A}}$$


$$I_2 = 1.5I_6 = 1.5 \times 10\text{ A} = \mathbf{15\text{ A}}$$

$$I_s = 3I_6 = 3 \times 10\text{ A} = \mathbf{30\text{ A}}$$


## 8.3 SOURCE Transformation



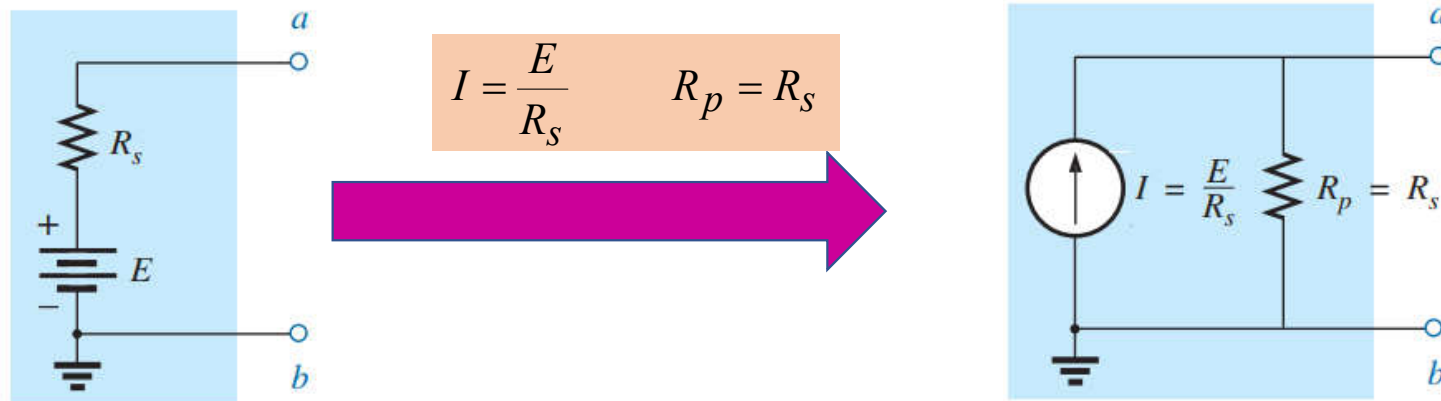
## Voltage Source Convert to Current Source



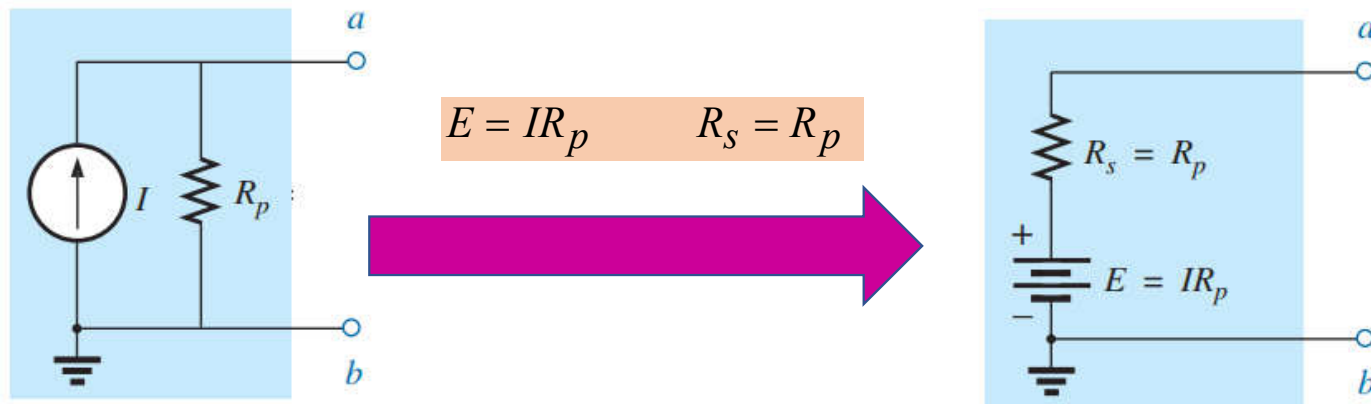
## Current Source Convert to Voltage Source



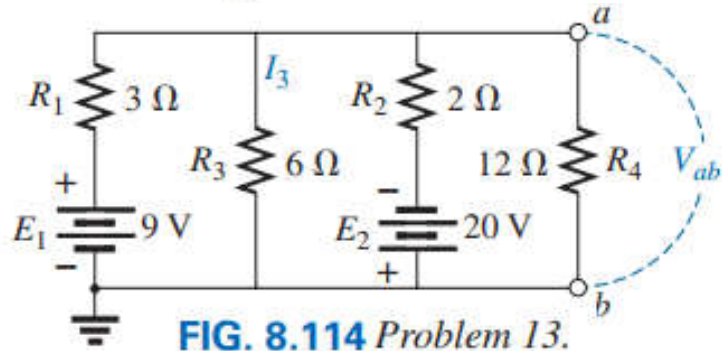
13. Convert the voltage sources in Fig. 8.114 to current sources.  
 a. Find the voltage  $V_{ab}$  and the polarity of points  $a$  and  $b$ .  
 b. Find the magnitude and direction of the current  $I_3$ .



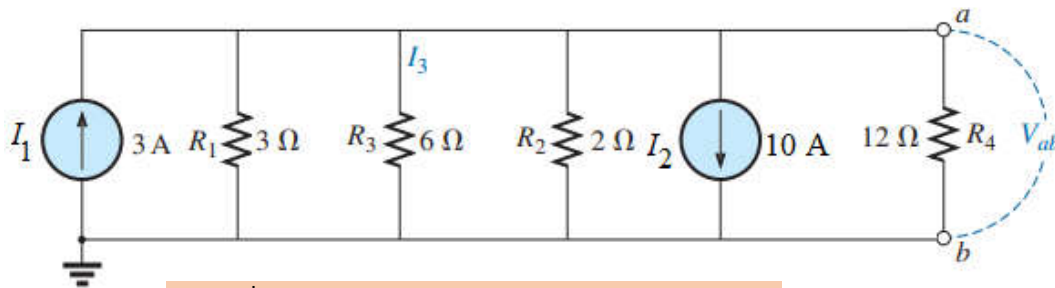
$$I_1 = \frac{E_1}{R_1} = \frac{9 \text{ V}}{3 \Omega} = 3 \text{ A} \quad I_2 = \frac{E_2}{R_2} = \frac{20 \text{ V}}{2 \Omega} = 10 \text{ A}$$


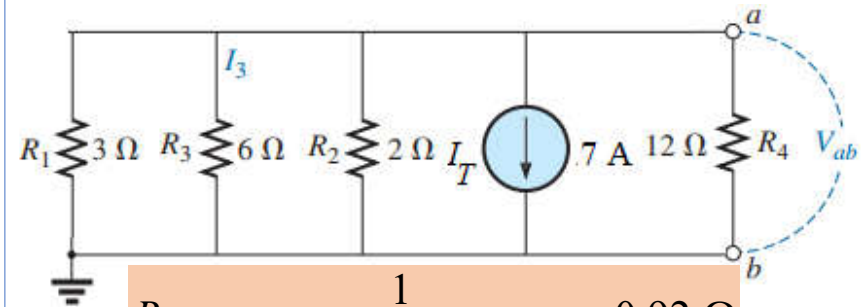
$$I_T \downarrow = I_2 - I_1 = 10 \text{ A} - 3 \text{ A} = 7 \text{ A}$$


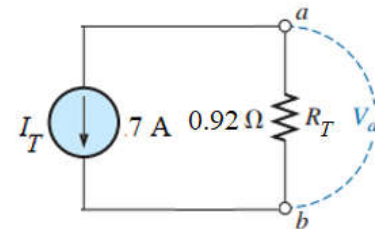
$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_6} + \frac{1}{R_2} + \frac{1}{R_4}} = 0.92 \Omega$$




$$V_{ab} = -I_T R_T = -6.44 \text{ V}$$

$$I_3 \uparrow = \frac{-V_{ab}}{R_3} = \frac{6.44 \text{ V}}{6 \Omega} = 1.07 \text{ A}$$


**Practice Book [Ch 8]**

**Problem: 7 ~ 10 and 14**

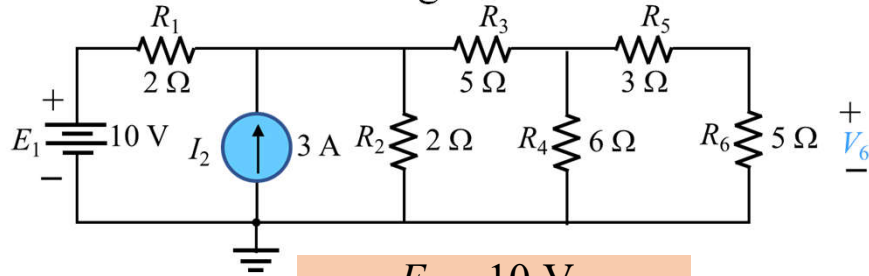**EXAMPLE 8.3.1** Using the source conversion find the value of voltage  $V_6$ .



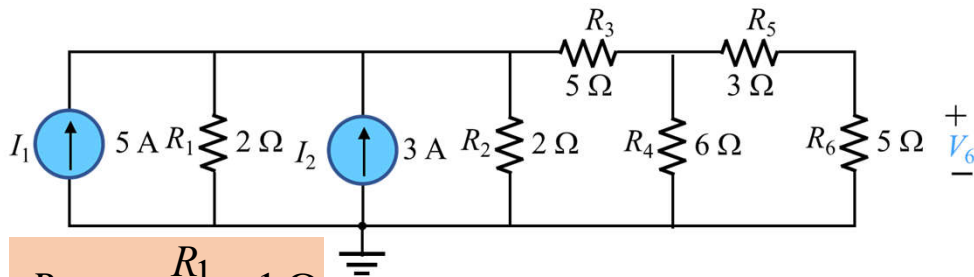
$$I_1 = \frac{E_1}{R_1} = \frac{10 \text{ V}}{2 \Omega} = 5 \text{ A}$$




$$R_{1//2} = \frac{R_1}{2} = 1 \Omega$$

$$I_3 = I_1 + I_2 = 8 \text{ A}$$

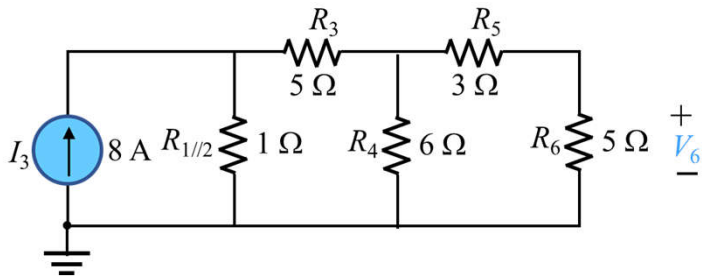


$$E_4 = I_3 R_{1//2} = 8 \text{ V}$$

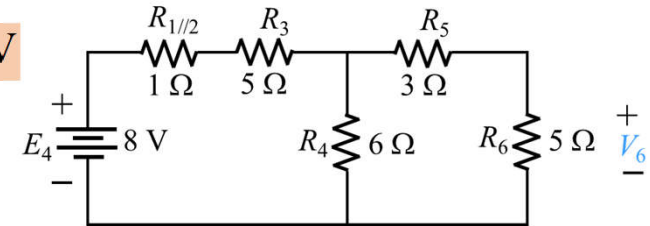


$$R_7 = R_{1//2} + R_3 = 6 \Omega$$
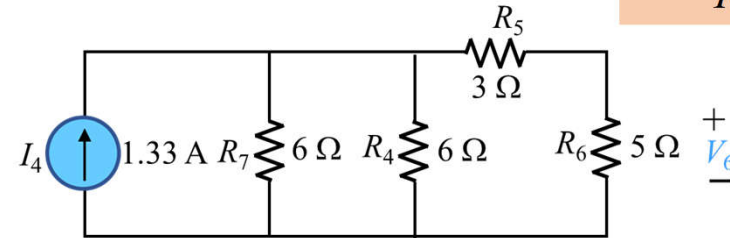
$$I_4 = \frac{E_4}{R_7} = 1.33 \text{ A}$$



$$R_{7//4} = \frac{R_7}{2} = 3 \Omega$$

$$E_5 = I_4 R_{7//4} = 4 \text{ V}$$

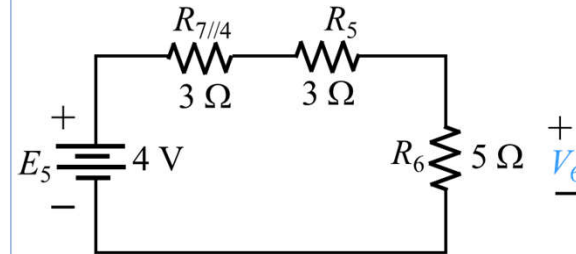

$$V_6 = \frac{R_6}{R_{7//4} + R_5 + R_6} E_5 = 1.1 \text{ V}$$





## More Examples Related to Series-Parallel Circuits




**Problem 12 [Ch 7]:** For the network in Fig. 7.72:

a. Determine the current  $I_1$ .

b. Calculate the currents  $I_2$  and  $I_3$ .

c. Determine the voltage levels  $V_a$  and  $V_b$ .

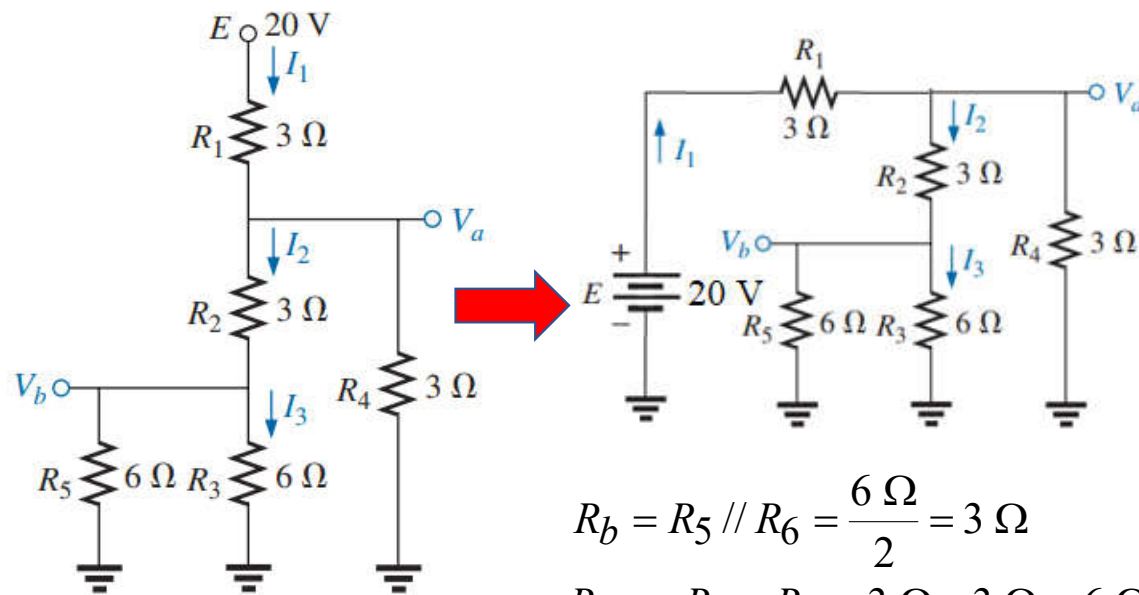

**FIG. 7.72**  
Problem 12.

$$R_b = R_5 // R_6 = \frac{6 \Omega}{2} = 3 \Omega$$

$$R_{b2} = R_b + R_2 = 3 \Omega + 3 \Omega = 6 \Omega$$

$$R_a = \frac{R_{b2} R_4}{R_{b2} + R_4} = 2 \Omega$$

$$R_T = R_1 + R_a = 3 \Omega + 2 \Omega = 5 \Omega$$

$$I_1 = \frac{E}{R_T} = \frac{20 \text{ V}}{5 \Omega} = 4 \text{ A}$$

$$V_a = \frac{R_a}{R_T} E = \frac{2 \Omega}{5 \Omega} \times 20 \text{ V} = 8 \text{ V}$$

$$I_2 = \frac{V_a}{R_{b2}} = \frac{8 \text{ V}}{6 \Omega} = 1.333 \text{ A}$$

$$V_b = I_2 R_b = 1.333 \text{ A} \times 3 \Omega \cong 4 \text{ V}$$

$$I_3 = \frac{V_b}{R_3} = \frac{I_2}{2} = \frac{1.333 \text{ A}}{2} = 0.667 \text{ A}$$

**Problem 10 [Ch 7]** Determine the unknown voltage ( $V$ ) and current ( $I$ ) for the following network.



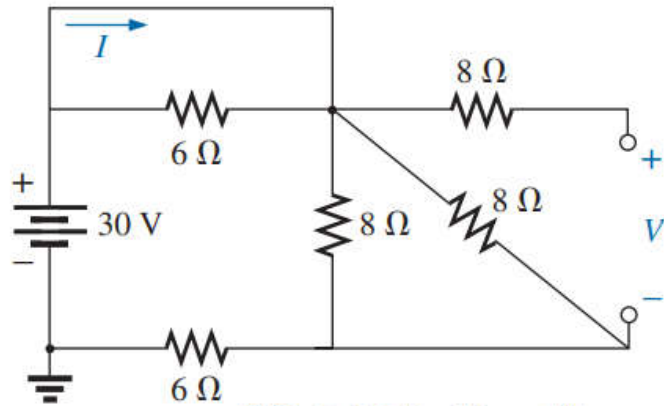
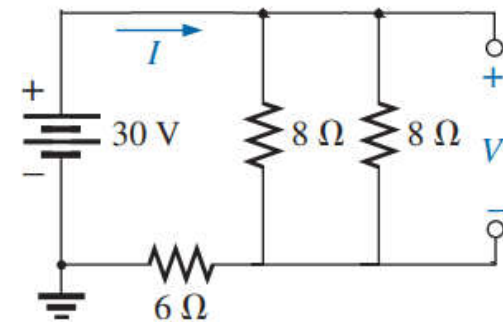


FIG. 7.78 Problem 18.

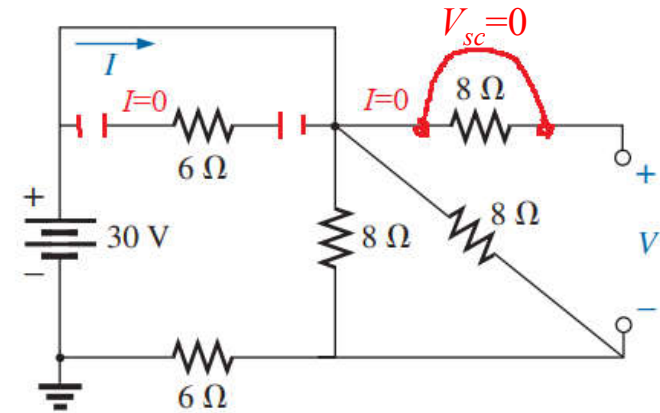
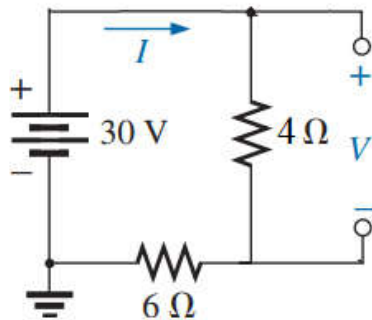
$$R_{8//8} = \frac{8\Omega}{2} = 4\Omega$$



$$I = \frac{30\text{ V}}{4\Omega + 6\Omega} = 3\text{ A}$$

$$V = 3\text{ A} \times 4\Omega = 12\text{ V}$$

**Problem 26** For the ladder network in Fig. 7.86: **a.** Determine  $R_T$ . **b.** Calculate  $I$ . **c.** Find  $I_8$ . **d.** Power consumed by  $R_6$  resistance. **e.** Power delivered by the 2 V supply.



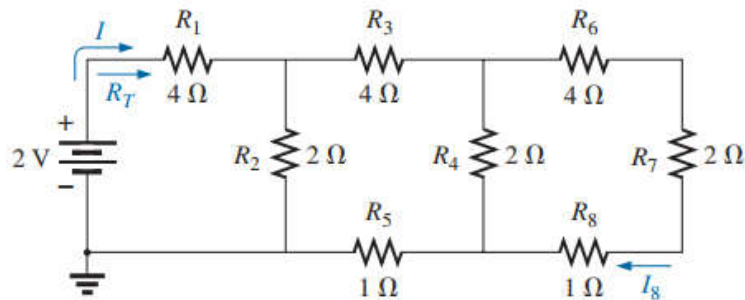


FIG. 7.86 Problem 26.


$$R_{s1} = R_6 + R_7 + R_8 = 7 \Omega$$

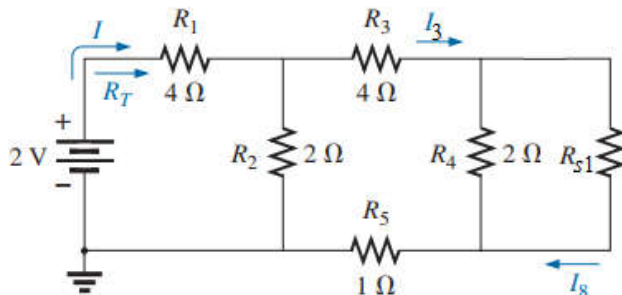
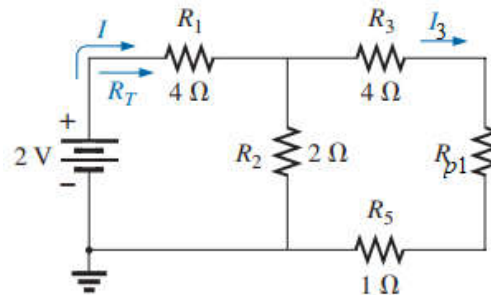
$$R_{p1} = \frac{R_{s1}R_4}{R_{s1} + R_4} = 1.56 \Omega$$


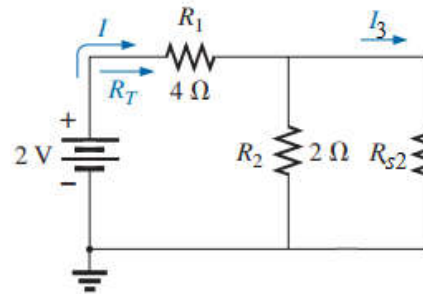
$$R_{s2} = R_3 + R_{p1} + R_5 = 6.56 \Omega$$



$$R_{p2} = \frac{R_{s2}R_2}{R_{s2} + R_2} = 1.53 \Omega$$

$$R_T = R_{p2} + R_1 = 5.53 \Omega$$

$$I = \frac{E}{R_T} = \frac{20 \text{ V}}{5.53 \Omega} = 361.66 \text{ mA}$$

$$I_3 = \frac{R_2}{R_2 + R_{s2}} I = 84.50 \text{ mA}$$

$$I_8 = \frac{R_4}{R_4 + R_{s1}} I_3 = 18.78 \text{ mA}$$

$$P_6 = I_8^2 R_6 = (18.78 \times 10^{-3})^2 \times 4 \Omega = 1.41 \text{ mW}$$

$$P_E = EI = (2 \text{ V}) \times (361.66 \times 10^{-3}) = 723.32 \text{ mW}$$

**Problem 28. [Ch. 7]** For the multiple ladder configuration in Fig. 7.88:

- a. Determine  $I$ . b. Calculate  $I_4$ . c. Find  $I_6$ . d. Find  $I_{10}$ .

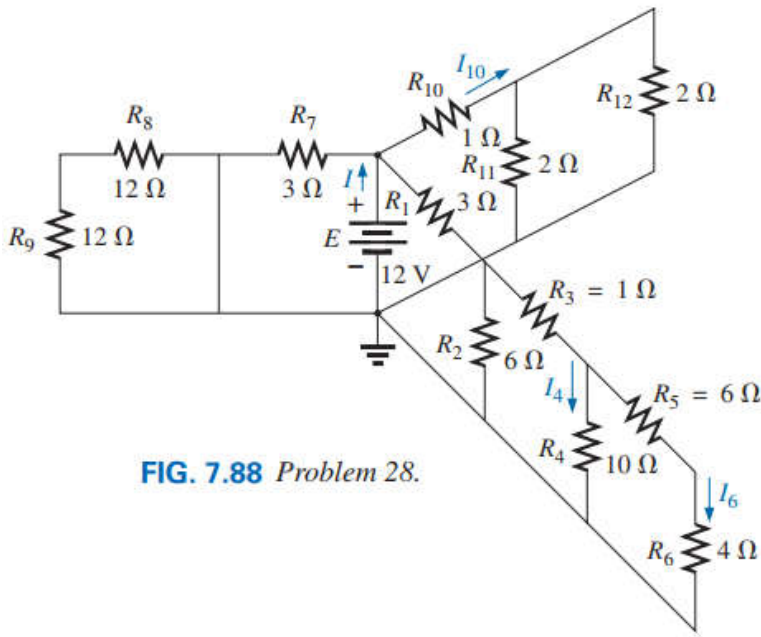


FIG. 7.88 Problem 28.

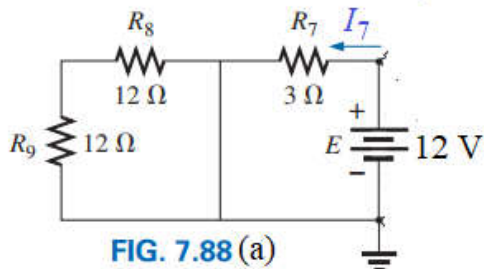


FIG. 7.88 (a)

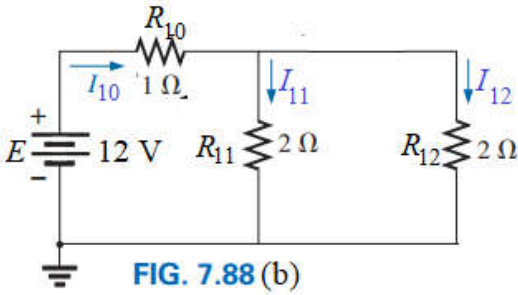


FIG. 7.88 (b)

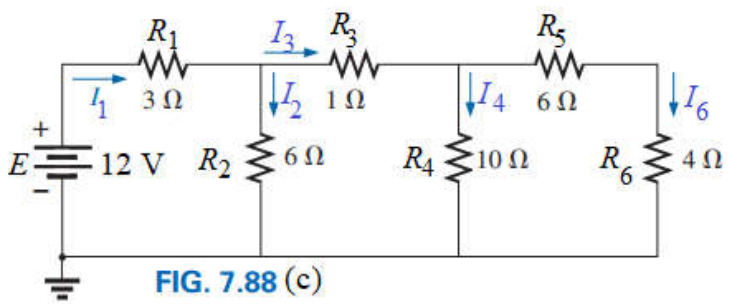


FIG. 7.88 (c)