



American International University- Bangladesh (AIUB)
Faculty of Engineering

Course Name: Introduction to Electrical Circuits
Semester: Fall 2022-23
Total Marks: 10
Faculty Name: Md. Ashiquzzaman

Course Code: COE 2101
Term: Mid
Submission Date: 26-10-2022
Assignment: 01

Course Outcome Mapping with Questions

Item	COs	POIs	K	P	A	Marks	Obtained Marks
Q1	CO2	P.a.2.C3	K2			2.5	
Q2	CO2	P.a.2.C3	K2			2.5	
Q3	CO2	P.a.2.C3	K2			2.5	
Q4	CO2	P.a.2.C3	K2			2.5	
Total:						10	

Student Information:

Student Name:	Student ID:
Section: H	Department:

Marking Rubrics (to be filled by Faculty):

	Excellent [2.5]	Proficient [2]	Good [1.5]	Acceptable [1]	Unacceptable [0.5]	No Response [0]	Secured Marks
Problem #	Detailed unique response explaining the concept properly and answer is correct with all works clearly shown.	Response with no apparent errors and the answer is correct, but explanation is not adequate/unique.	Response shows understanding of the problem, but the final answer may not be correct	Partial problem is solved; response indicates part of the problem was not understood clearly.	Unable to clarify the understanding of the problem and method of the problem solving was not correct	No Response/(Copied/identical submissions will be graded as 0 for all parties concerned)	
1							
2							
3							
4							
Comments						Total marks (10)	

1. Applying superposition theorem, find the current I through the 10 ohm resistor for the network in Fig. 1

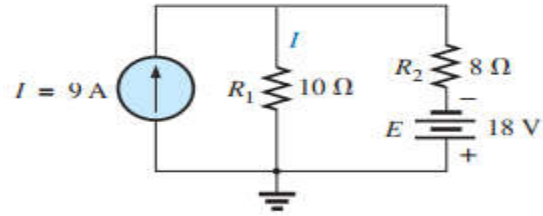


Fig. 1

2. Modify the following network in Fig. 2 as the Thévenin equivalent circuit for the network external to the resistor R .

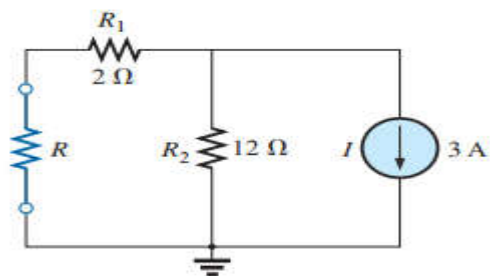


Fig. 2

3. Modify the following network in Fig. 3 as the Norton equivalent circuit for the network external to the resistor R .

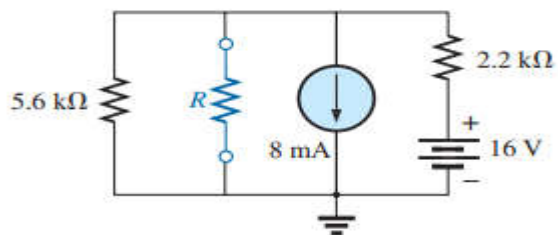


Fig. 3

4. For the network in Fig. 4, calculate the value of R for maximum power to R and calculate the maximum power to R by applying maximum power transfer theorem.

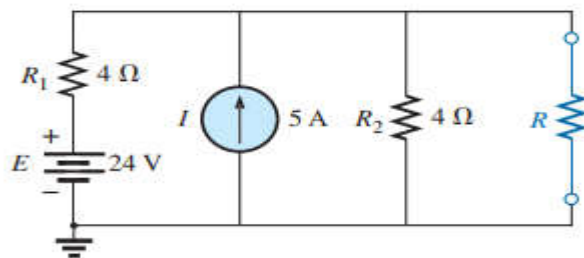


Fig. 4